

Electricity & Magnetism

Lecture 9: Electric Current

Today's Concept:

Electric Current

How do you feel about circuits



- A) I completely understand them from high school
- B) Need Review
- C) Still hopeless
- D) Circuit? What's that?

Your stuff

- so which way does DC current flow? - _ -
- “How many different things will sigma symbolize???”
- “Since $R = \rho L/A$, the greater the cross sectional area, the smaller the resistance, but the greater the length the higher the resistance. Is that why long cables have to be very thick?”
- “What if I put ammeter right between + and -?”
- “the part relating to the ohm's law and current density stuff makes no sense to me.”

A Big Idea Review

Coulomb's Law

Force law between point charges

$$\vec{F}_{1,2} = \frac{kq_1q_2}{r_{1,2}^2} \hat{r}_{1,2}$$



Electric Field

Force per unit charge

$$\vec{E} \equiv \frac{\vec{F}}{q}$$

Electric Field

Property of Space
Created by Charges
Superposition

Gauss' Law

Flux through closed surface is always proportional to charge enclosed

$$\oint_{\text{surface}} \vec{E} \cdot \vec{A} = \frac{Q_{\text{enclosed}}}{\epsilon_0}$$

Gauss' Law

Can be used to determine E field



Spheres
Cylinders
Infinite Planes

Electric Potential

Potential energy per unit charge

$$\Delta V_{a \rightarrow b} \equiv \frac{\Delta U_{a \rightarrow b}}{q} = - \int_a^b \vec{E} \cdot d\vec{l}$$

Capacitance

Relates charge and potential for two conductor system

$$C \equiv \frac{Q}{V}$$

Electric Potential

Scalar Function that can be used to determine E

$$\vec{E} = -\vec{\nabla} V$$

A Note on Units

- ★ Force is newtons: $N = \text{kg} \cdot \text{m}/\text{s}^2$
- ★ Electric Field: newton/coulomb ($N/C = V/m$)
- ★ Electric potential: newton-meter/coulomb = volt
 - $\text{kg} \cdot \text{m}^2/\text{s}^2\text{C} = V$
- ★ Capacitance: farad = coulomb/volt
 - farad is **big**, we usually use
 - $\mu\text{F} = 10^{-6} \text{ F}$
 - $\text{pF} = 10^{-12} \text{ F}$ ($\mu\mu\text{F}$ in olden days, “puffs” now)
 - ($\text{nF} = 10^{-9}$ not customary in N. America)

Applications of Big Ideas

Conductors
Charges free to move



What Determines
How They Move?




They move until
 $E = 0$!




$E = 0$ in conductor
determines charge
densities on surfaces

Spheres
Cylinders
Infinite Planes

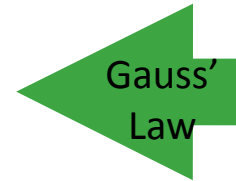

Field Lines &
Equipotentials

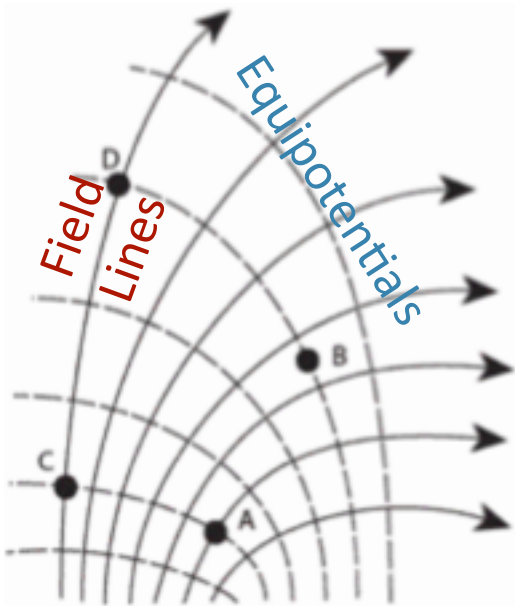


Work Done By E Field

$$W_{a \rightarrow b} = \int_a^b \vec{F} \cdot d\vec{l} = \int_a^b q\vec{E} \cdot d\vec{l}$$

Change in Potential Energy

$$\Delta V_{a \rightarrow b} \equiv \frac{\Delta U_{a \rightarrow b}}{q} = - \int_a^b \vec{E} \cdot d\vec{l}$$

Capacitor Networks

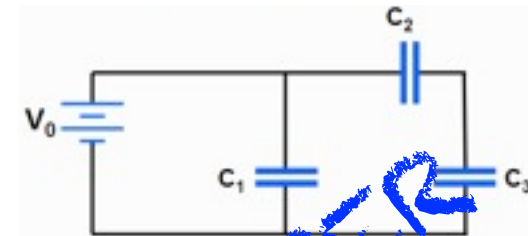

Series:
 $(1/C_{23}) = (1/C_2) + (1/C_3)$


Parallel
 $C_{123} = C_1 + C_{23}$

Key Concepts:

- 1) How resistance depends on A, L, σ, ρ σ is **conductivity** here (not surface charge density)
 ρ is **resistivity** here (not volume charge density).
- 2) How to combine resistors in series and parallel
- 3) Understanding resistors in circuits

Today's Plan:

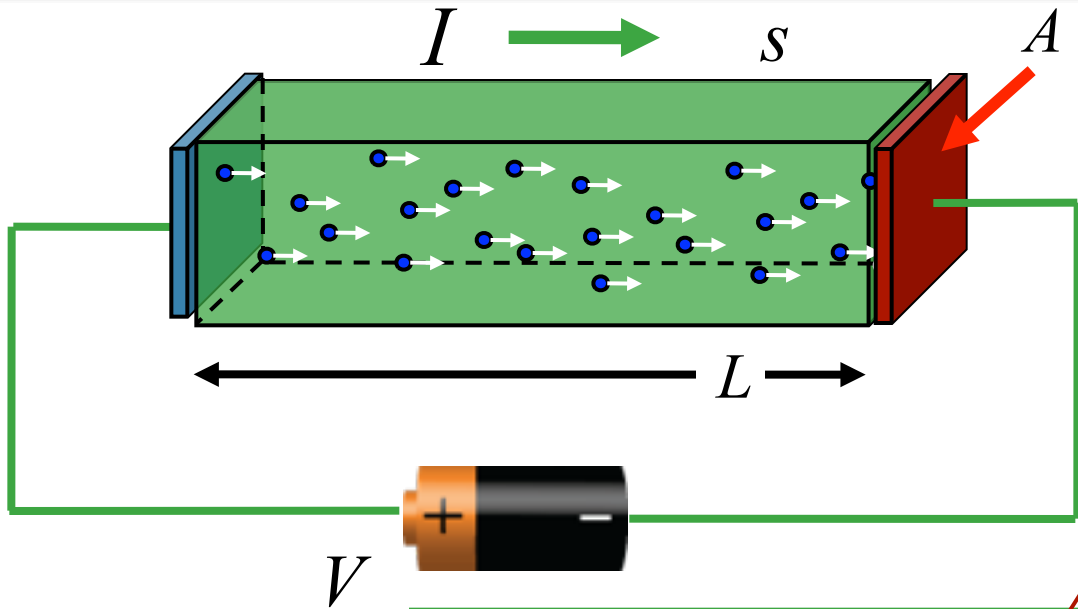- 1) Review of resistance & preflights
- 2) Work out a circuit problem in detail



Conductivity – high for good conductors.

$$\text{Ohm's Law: } J = \sigma E$$

Observables:

$$V = EL$$

$$I = JA$$



$$I/A = \sigma V/L$$



$$I = V/(L/\sigma A)$$



$R = \text{Resistance}$

$$\rho = 1/\sigma$$

$$I = V/R$$



$$R = \frac{L}{\sigma A}$$

This is just like Plumbing!

I is like flow rate of water

V is like pressure

R is how hard it is for water to flow in a pipe

$$R = \frac{L}{\sigma A}$$


To make R big, make L long or A small



To make R small, make L short or A big



1 CheckPoint: Two Resistors 2

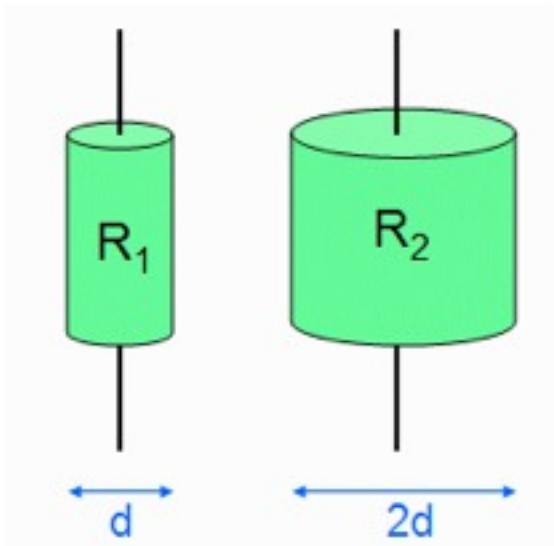


- A) $V_1 > V_2$ B) $V_1 = V_2$ C) $V_1 < V_2$

Same current through both resistors

Compare voltages across resistors


$$R \propto \frac{L}{A}$$

$$V = IR \propto \frac{L}{A}$$

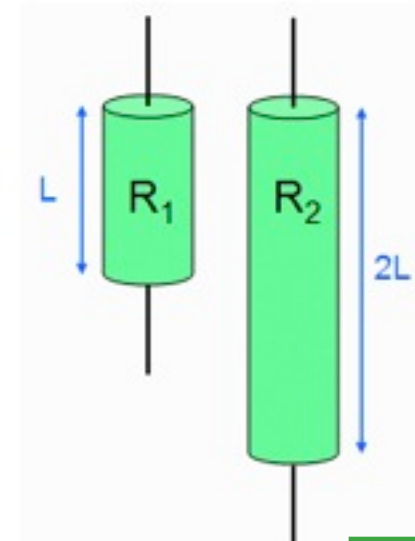


- A) $V_1 > V_2$ B) $V_1 = V_2$ C) $V_1 < V_2$

Two Resistors: Question 1 (N = 23)

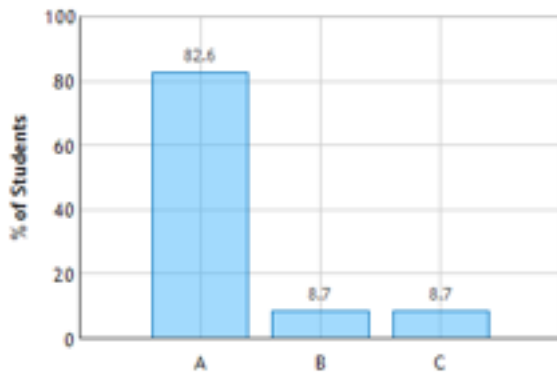

$$A_2 = 4A_1 \Rightarrow V_2 = \frac{1}{4}V_1$$


Two Resistors: Question 3 (N = 23)

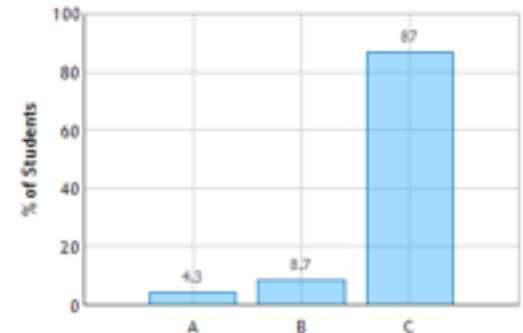


$$L_2 = 2L_1 \Rightarrow V_2 = 2V_1$$

CheckPoint: Current Density


The SAME amount of current I passes through three different resistors. R_2 has twice the cross-sectional area and the same length as R_1 , and R_3 is three times as long as R_1 but has the same cross-sectional area as R_1 . In which case is the CURRENT DENSITY through the resistor the smallest?

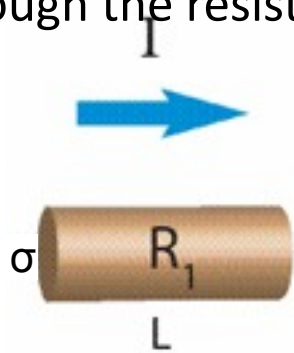

Case 1

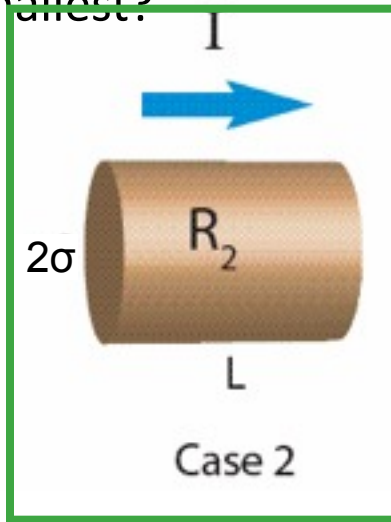

Case 2

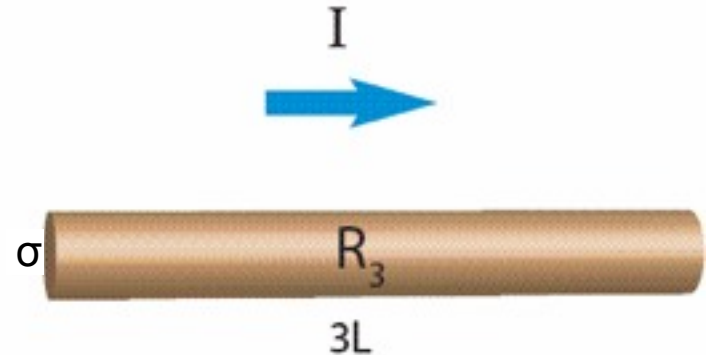


Case 3

$$J \equiv \frac{I}{A} \quad \longrightarrow \quad J_1 = J_3 = 2J_2$$


Same Current $\longrightarrow J \propto \frac{1}{A}$

Resistor Network: Question 1 (N = 23)

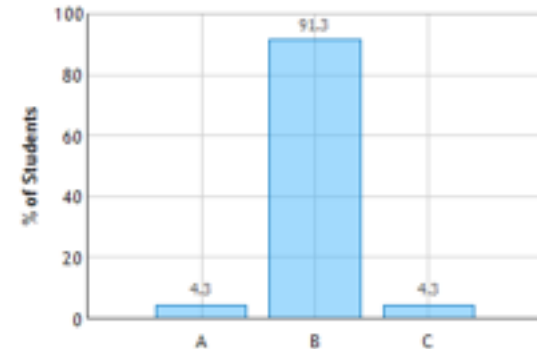

Resistor Summary

Series

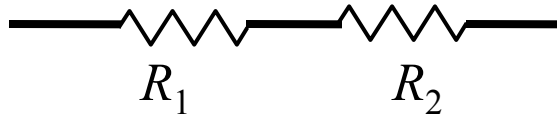

Wiring

Each resistor on the same wire.

Voltage

Different for each resistor.

$$V_{total} = V_1 + V_2$$

Voltage Divider

Current

Same for each resistor


$$I_{total} = I_1 = I_2$$

Resistance

Increases

$$R_{eq} = R_1 + R_2$$

Parallel

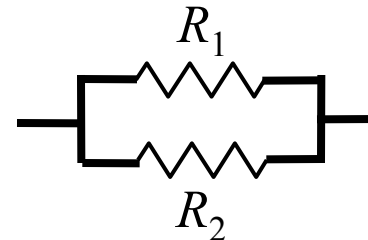

Each resistor on a different wire.

Same for each resistor.

$$V_{total} = V_1 = V_2$$

Different for each resistor

$$I_{total} = I_1 + I_2$$

Current Divider

Decreases

$$1/R_{eq} = 1/R_1 + 1/R_2$$

Symbols

★ Resistor symbol (ANSI)

- N. America, Japan, China(?)



4.7 k = 4700 ohm

1.8 Ω = 1.8 ohm

★ Alternate resistor symbol (DIN)


- Europe, Middle East, Aus/NZ, Africa(?)



4k7 = 4700 ohm

1R8 = 1.8 ohm

★ Voltage Source

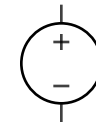

★ Electrochemical Cell (“battery”)

sometimes used for voltage source



CheckPoint: Resistor Network 1



Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.

Compare the current through R_2 with the current through R_3 :

A. $I_2 > I_3$

B. $I_2 = I_3$

C. $I_2 < I_3$

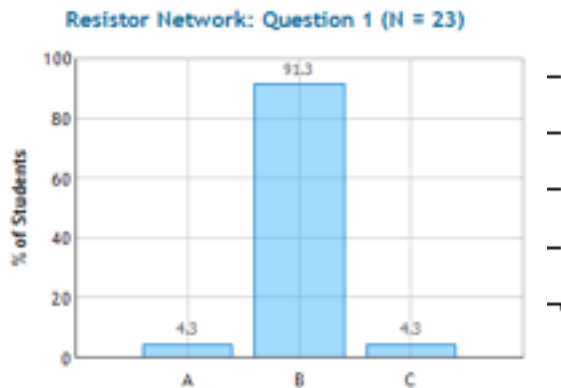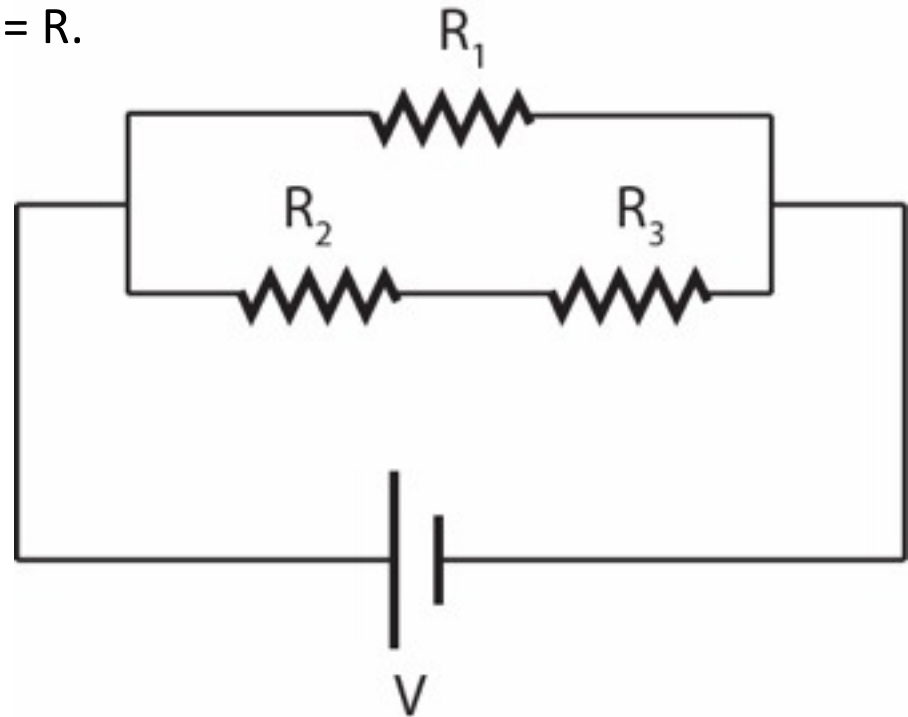


R_2 in series with R_3



Current through R_2 and R_3 is the same

$$I_{23} = \frac{V}{R_2 + R_3}$$

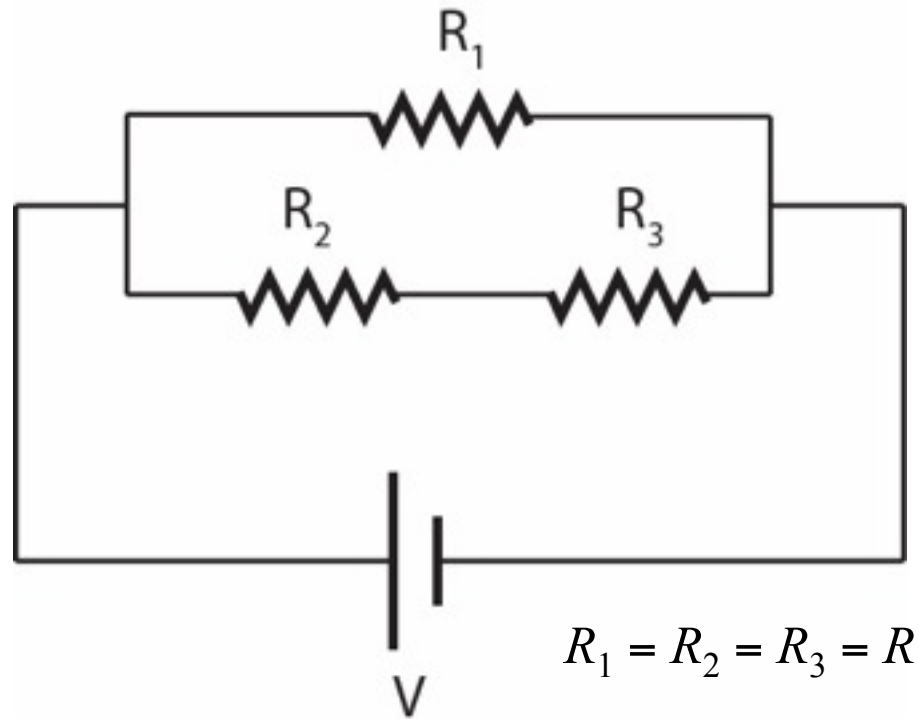

CheckPoint 2

Compare the current through R_1
with the current through R_2

$$I_1 \longleftrightarrow I_2$$

CheckPoint 3

Compare the voltage across R_2
with the voltage across R_3

$$V_2 \longleftrightarrow V_3$$


CheckPoint 4

Compare the voltage across R_1
with the voltage across R_2

$$V_1 \longleftrightarrow V_2$$

CheckPoint: Resistor Network 2

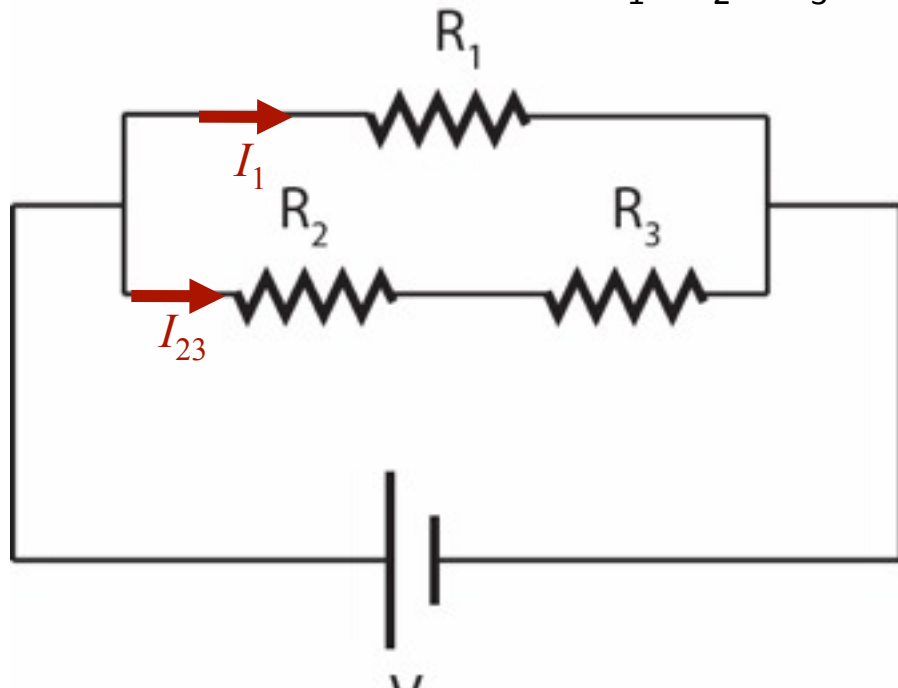Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.



Compare the current through R_1 with the current through R_2 :

A. $I_1/I_{23}=1/2$


B. $I_1/I_{23}=1/3$

C. $I_1 = I_{23}$

D. $I_1/I_{23}=2$

E. $I_1/I_{23}=3$

Resistor Network: Question 2 (N = 23)

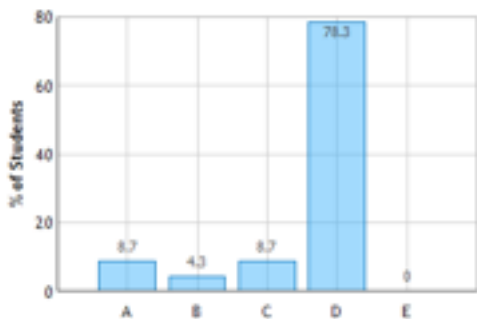

We know:

$$I_{23} = \frac{V}{R_2 + R_3}$$

Similarly:


$$I_1 = \frac{V}{R_1}$$

$$I_1 = I_{23} \frac{R_2 + R_3}{R_1}$$

$$\frac{I_1}{I_{23}} = \frac{R_2 + R_3}{R_1} = 2$$

CheckPoint: Resistor Network 3

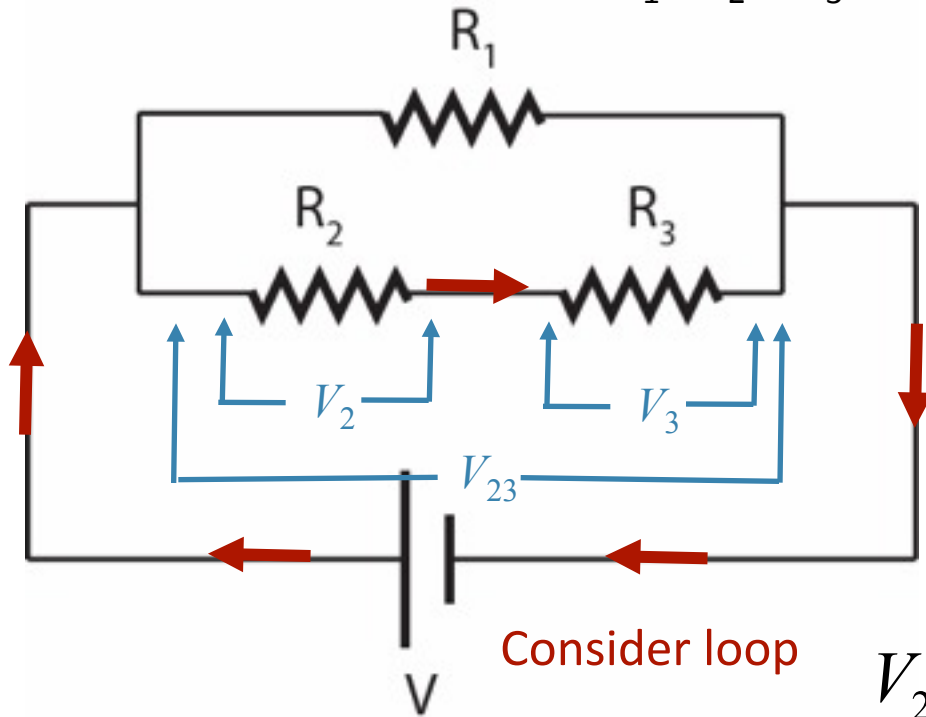Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.



Compare the voltage across R_2 with the voltage across R_3 :


- A. $V_2 > V_3$
- B. $V_2 = V_3 = V$
- C. $V_2 = V_3 < V$
- D. $V_2 < V_3$

$$V_{23} = V$$

$$V_{23} = V_2 + V_3 \quad \longrightarrow \quad V_2 = V_3 = \frac{V}{2}$$


$$R_2 = R_3 \Rightarrow V_2 = V_3$$

Resistor Network: Question 4 (N = 23)

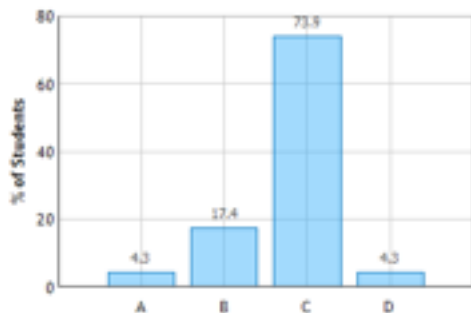

CheckPoint: Resistor Network 4

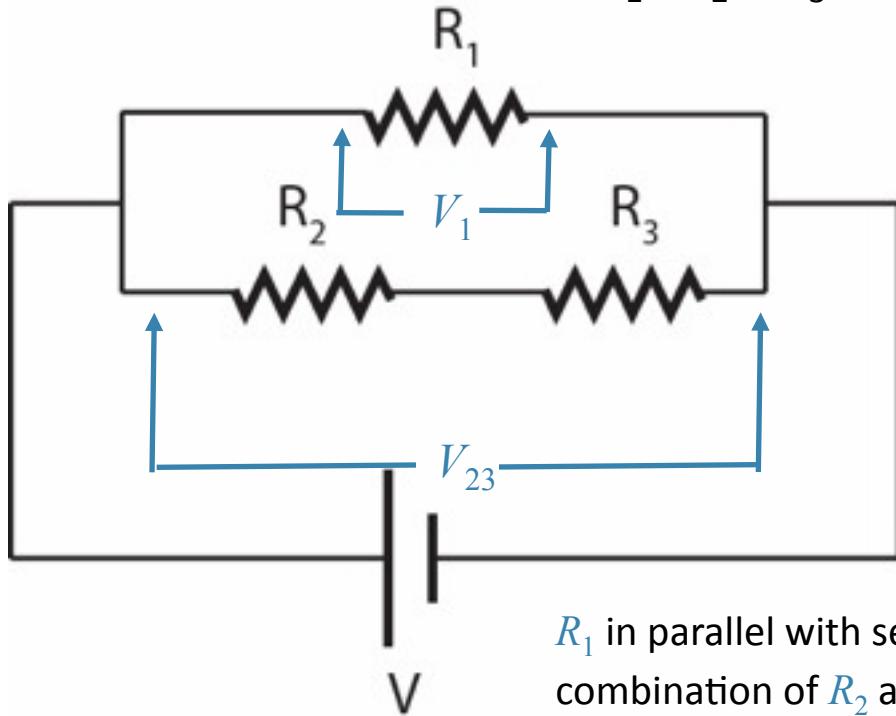Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.




Compare the voltage across R_1 with the voltage across R_2 .

- A. $V_1 = V_2 = V$
- B. $V_1 = 1/2 V_2 = V$
- C. $V_1 = 2V_2 = V$
- D. $V_1 = 1/2 V_2 = 1/5 V$
- E. $V_1 = 1/2 V_2 = 1/2 V$

R_1 in parallel with series combination of R_2 and R_3

Resistor Network: Question 5 (N = 23)

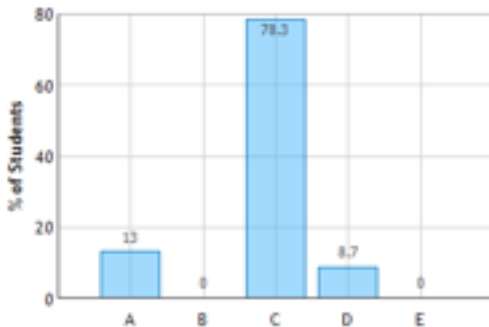


$$V_1 = V_{23}$$

$$R_2 = R_3 \Rightarrow V_2 = V_3 \longrightarrow V_1 = 2V_2 = V$$

$$V_{23} = V_2 + V_3 = 2V_2$$

Calculation

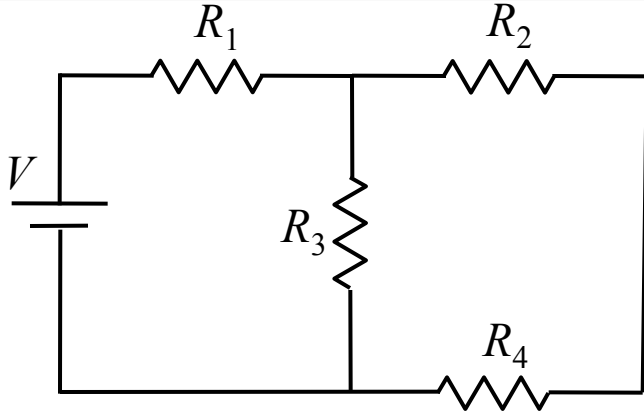

In the circuit shown: $V = 18V$,

$R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?

Conceptual Analysis:

Ohm's Law: when current I flows through resistance R , the potential drop V is given by:

$$V = IR.$$

Resistances are combined in series and parallel combinations

$$R_{series} = R_a + R_b$$

$$(1/R_{parallel}) = (1/R_a) + (1/R_b)$$


Strategic Analysis:

Combine resistances to form equivalent resistances

Evaluate voltages or currents from Ohm's Law

Expand circuit back using knowledge of voltages and currents

Calculation

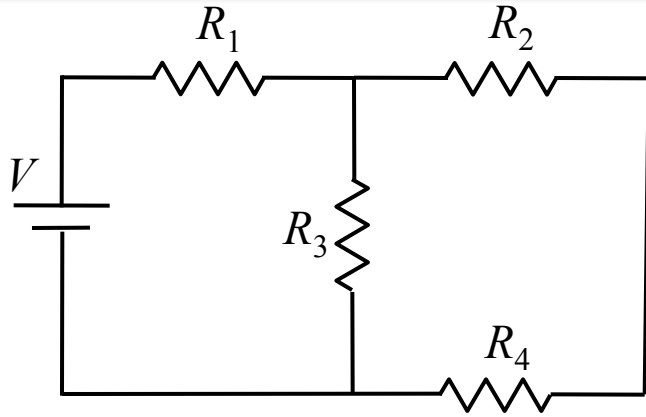

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?

Combine Resistances:


R_1 and R_2 are connected:

A) in series

B) in parallel

C) neither in series nor in parallel

Parallel Combination

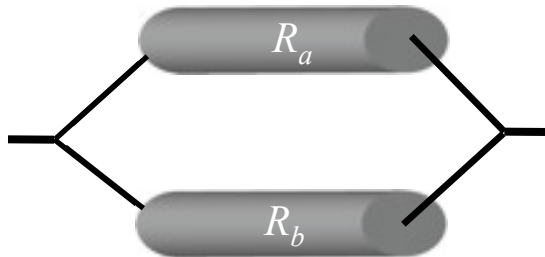


Parallel: Can make a loop that contains only those two resistors

Series Combination



Series : Every loop with resistor 1 also has resistor 2.

Calculation

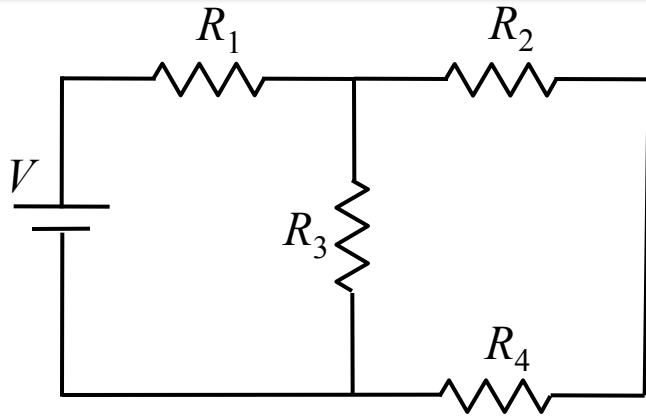

In the circuit shown: $V = 18V$,

$R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.


What is V_2 , the voltage across R_2 ?

We first will combine resistances $R_2 + R_3 + R_4$:

Which of the following is true?

- A) R_2 , R_3 and R_4 are connected in series
- B) R_2 , R_3 , and R_4 are connected in parallel
- C) R_3 and R_4 are connected in series (R_{34}) which is connected in parallel with R_2
- D) R_2 and R_4 are connected in series (R_{24}) which is connected in parallel with R_3
- E) R_2 and R_4 are connected in parallel (R_{24}) which is connected in parallel with R_3

Calculation

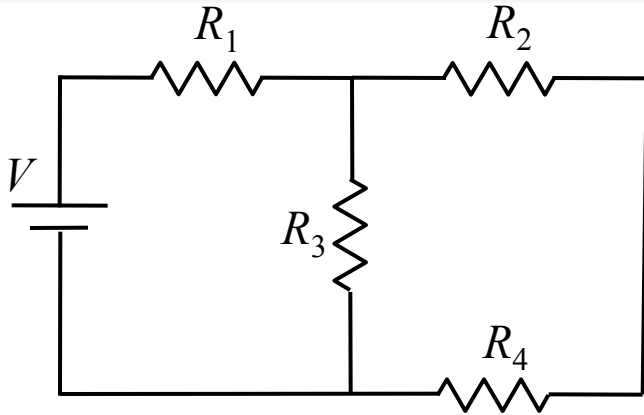


In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.


What is V_2 , the voltage across R_2 ?

R_2 and R_4 are connected in series (R_{24}) which is connected in parallel with R_3

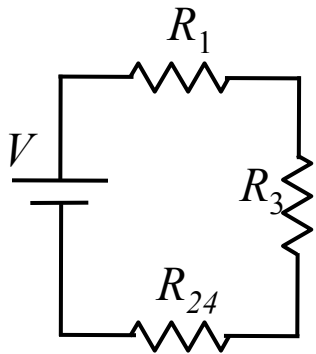
Redraw the circuit using the equivalent resistor $R_{24} =$ series combination of R_2 and R_4 .



(A)

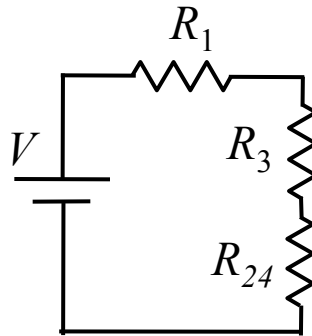


(B)

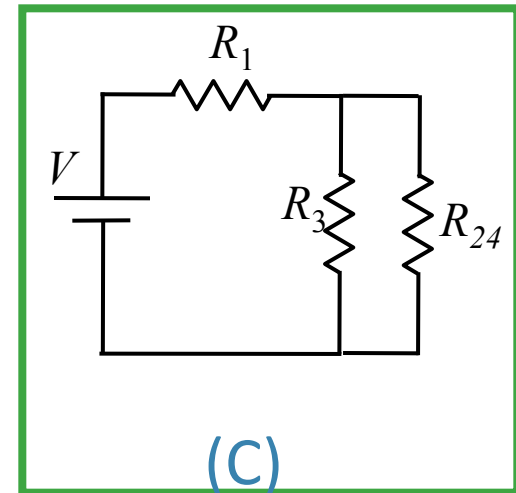

(C)

Calculation

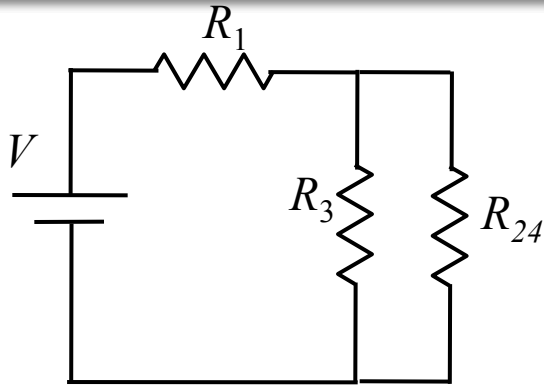

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?

Combine Resistances:

R_2 and R_4 are connected in series = R_{24}

R_3 and R_{24} are connected in parallel = R_{234}


What is the value of R_{234} ?

- A) $R_{234} = 1\Omega$ **B) $R_{234} = 2\Omega$** C) $R_{234} = 4\Omega$ D) $R_{234} = 6\Omega$

R_2 and R_4 in series $\rightarrow R_{24} = R_2 + R_4 = 2\Omega + 4\Omega = 6\Omega$

$(1/R_{parallel}) = (1/R_a) + (1/R_b) \rightarrow 1/R_{234} = (1/3) + (1/6) = (3/6)\Omega^{-1} \rightarrow R_{234} = 2\Omega$

Calculation

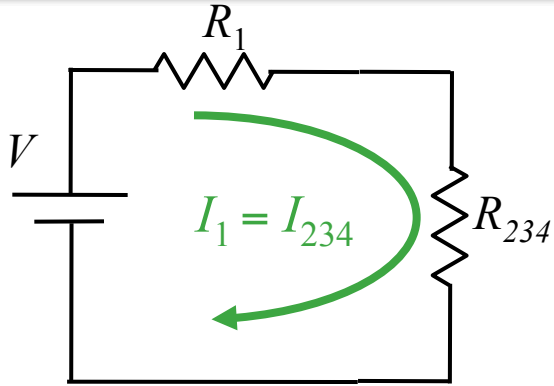


In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

$$R_{24} = 6\Omega \quad R_{234} = 2\Omega$$

What is V_2 , the voltage across R_2 ?

R_1 and R_{234} are in series. $R_{1234} = 1 + 2 = 3\Omega$


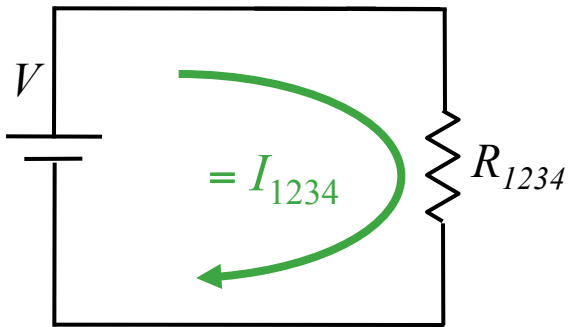
Our next task is to calculate the total current in the circuit



Ohm's Law tells us: $I_{1234} = V/R_{1234}$

$$= 18 / 3$$
$$= 6 \text{ Amps}$$

Calculation

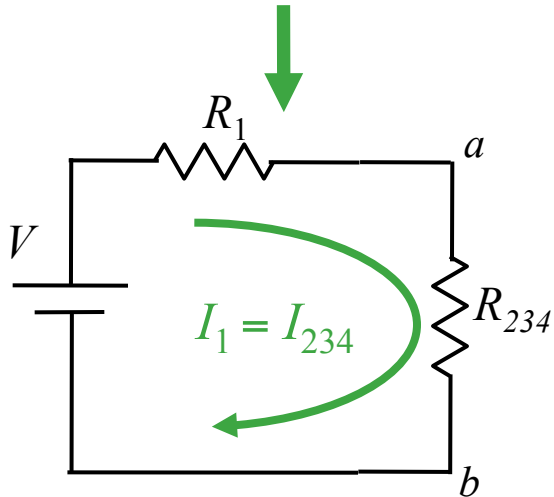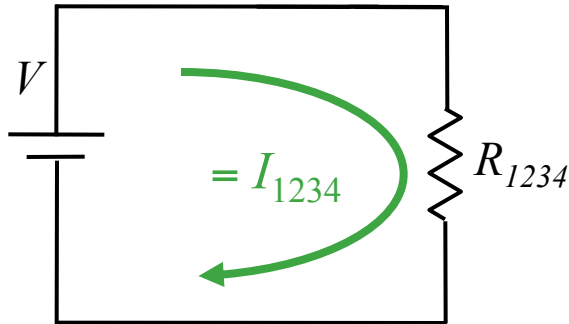

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

$$R_{24} = 6\Omega \quad R_{234} = 2\Omega \quad I_{1234} = 6A$$

What is V_2 , the voltage across R_2 ?

$$I_{234} = I_{1234} \quad \text{Since } R_1 \text{ in series with } R_{234}$$

$$\begin{aligned} V_{234} &= I_{234} R_{234} \\ &= 6 \times 2 \\ &= 12 \text{ Volts} \end{aligned}$$

What is V_{ab} , the voltage across R_{234} ?

A) $V_{ab} = 1V$



B) $V_{ab} = 2V$

C) $V_{ab} = 9V$

D) $V_{ab} = 12V$

E) $V_{ab} = 16V$

Calculation

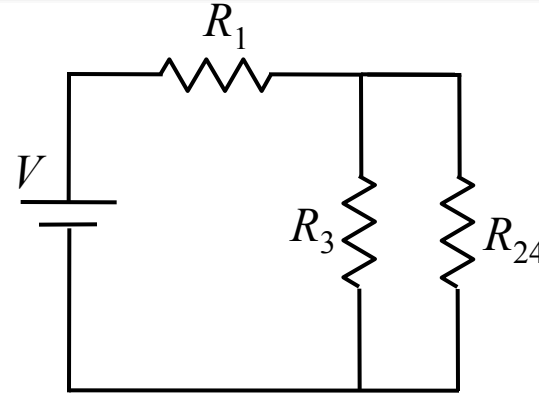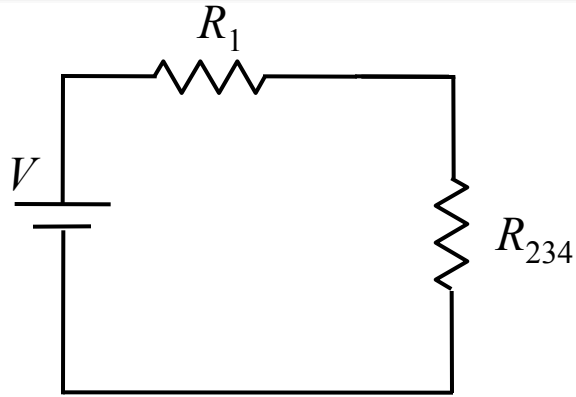

$$V = 18V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$R_4 = 4\Omega$$

$$R_{24} = 6\Omega$$

$$R_{234} = 2\Omega$$

$$I_{1234} = 6 \text{ Amps}$$

$$I_{234} = 6 \text{ Amps}$$

$$V_{234} = 12V$$

Which of the following are true?

A) $V_{234} = V_{24}$

B) $I_{234} = I_{24}$

C) Both A+B

D) None

R_3 and R_{24} were combined in parallel to get R_{234}

Voltages are same! What is V_2 ?



Ohm's Law

$$I_{24} = V_{24} / R_{24}$$

$$= 12 / 6$$

$$= 2 \text{ Amps}$$

Calculation

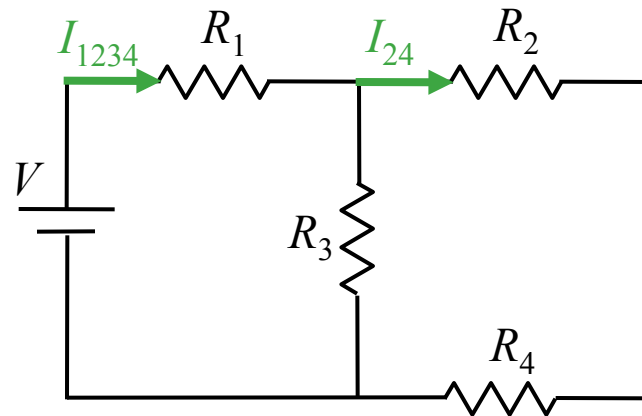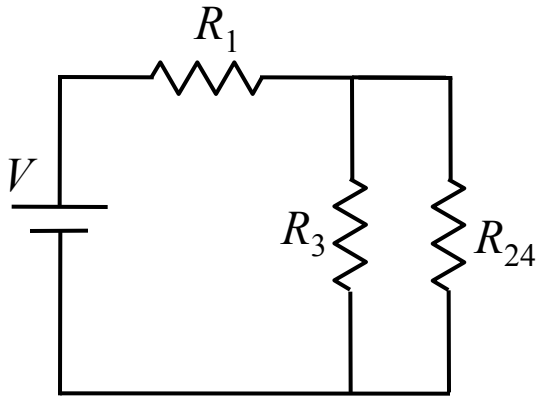

Which of the following are true?

- A) $V_{24} = V_2$ **B) $I_{24} = I_2$** C) Both A+B D) None

R_2 and R_4 where combined in series to get R_{24} → Currents are same!

Ohm's Law

$$\begin{aligned} V_2 &= I_2 R_2 \\ &= 2 \times 2 \\ &= 4 \text{ Volts!} \end{aligned}$$

The Problem Can Now Be Solved!

$$V = 18V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$R_4 = 4\Omega.$$

$$R_{24} = 6\Omega$$

$$R_{234} = 2\Omega$$

$$I_{1234} = 6 \text{ Amps}$$

$$I_{234} = 6 \text{ Amps}$$


$$V_{234} = 12V$$

$$V_{24} = 12V$$

$$I_{24} = 2 \text{ Amps}$$

What is V_2 ?

Quick Follow-Ups

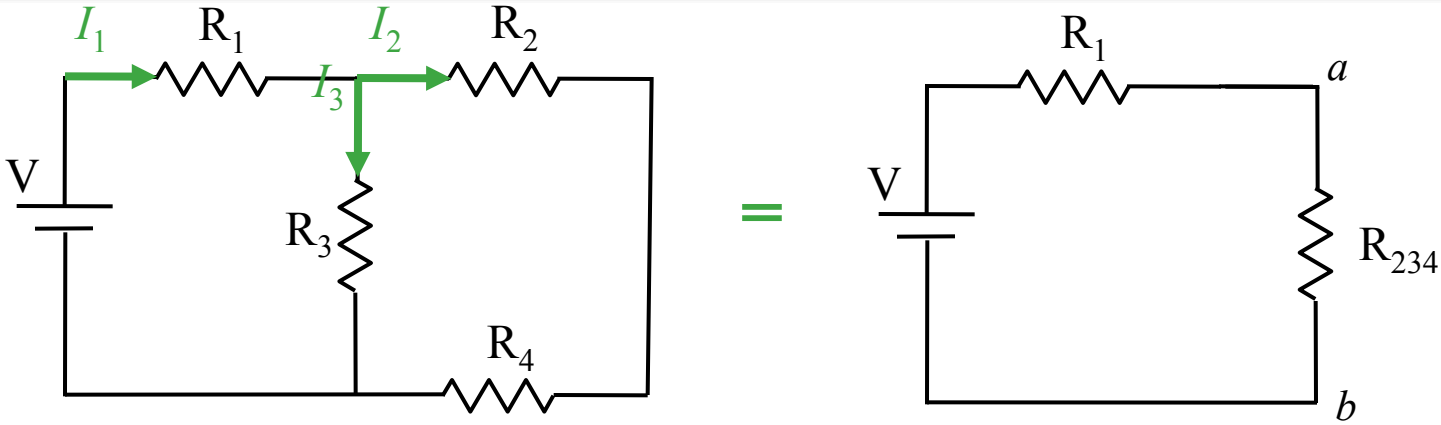

- $V = 18V$
- $R_1 = 1\Omega$
- $R_2 = 2\Omega$
- $R_3 = 3\Omega$
- $R_4 = 4\Omega$
- $R_{24} = 6\Omega$
- $R_{234} = 2\Omega$
- $V_{234} = 12V$
- $V_2 = 4V$
- $I_{1234} = 6 \text{ Amps}$

What is I_3 ?

- A) $I_3 = 2 A$
- B) $I_3 = 3 A$
- C) $I_3 = 4 A$**

$V_3 = V_{234} = 12V \rightarrow I_3 = V_3/R_3 = 12V/3\Omega = 4A$

What is I_1 ?

We know $I_1 = I_{1234} = 6 A$

NOTE: $I_2 = V_2/R_2 = 4/2 = 2 A \rightarrow I_1 = I_2 + I_3$ Make Sense?