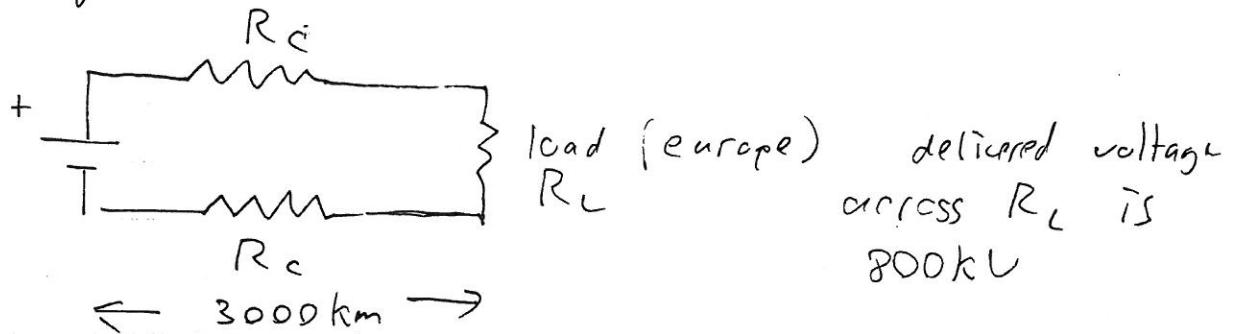


Assignment #15 Physics 346

① Equivalent circuit:



delivered voltage across R_L is 800 kV

(a) Delivered power across R_L is $5 \times 10^9 \text{ W}$
delivered voltage across R_L is 800 kV

$$\therefore \text{current through } R_L \text{ is } \frac{P_{\text{delivered}}}{V_{\text{delivered}}} = \frac{5 \times 10^9 \text{ W}}{8 \times 10^5 \text{ V}}$$

$$\therefore I = 6250 \text{ A}$$

There are 2 cables each having resistance R_c

Power lost to cables is $I^2(2R_c)$ (2 cables)

We need $I^2(2R_c) < 5 \times 10^8 \text{ W}$ (10% of delivered power)

$$\therefore R_c < \frac{5 \times 10^8 \text{ W}}{(6250 \text{ A})^2 2} = \underline{\underline{6.4 \Omega}}$$

$$R_c = \rho \frac{L}{A} = \rho \frac{L}{\pi (D/2)^2} \quad \text{where } D = \text{cable diameter}$$

$$\text{Rearrange } D = 2 \sqrt{\frac{\rho L}{\pi \rho R_c}} = 2 \sqrt{\frac{(1.72 \times 10^{-8} \Omega \text{ m})(5 \times 10^6 \text{ m})}{\pi 6.4 \Omega}}$$

$$\therefore \text{Must have } D \geq \underline{\underline{10 \text{ cm}}}$$

- 2 -

(b) What voltage must be generated in Africa?

Voltage dropped across each wire is

$$V_c = IR_c$$

$$\text{total voltage dropped is } 2V_c = 2IR_c \\ = 2(6250A)(6.4\Omega)$$

$$= 80,000V$$

∴ Voltage in Africa must be 880,000V

(old midterm question)

(2)

An electric car requires 15 kWh of electrical energy to travel 100 km. The car must have a design range of 300 km. It is designed to run on Pb acid batteries which have a voltage of 12 V and a capacity of 90 A-hr.

(a) (2 marks) What is the total stored charge required to achieve this range?

$$\text{Total energy } E = 15 \text{ kWh} \times 3 = 45 \text{ kWh} = VQ$$
$$= 1.62 \times 10^8$$
$$\therefore Q = \frac{E}{V} = \frac{(45 \text{ kWh})(3.6 \times 10^6 \text{ J/kWh})}{(12 \text{ V})}$$
$$= 1.35 \times 10^7 \text{ C} \times \frac{1 \text{ A} \cdot \text{h}}{3600 \text{ s}} = 3.75 \times 10^3 \text{ Ah}$$

(b) (1 mark) how many batteries will be necessary to achieve this range?

$$\# \text{ of batteries} = \frac{3.75 \times 10^3 \text{ Ah}}{90 \text{ Ah/batt.}} = \underline{\underline{42 \text{ batt.}}}$$

8. Microwave radiation from a cell phone with a wavelength of 16 cm is incident on a surface with an intensity of 0.01 W/cm².

(a) (2 marks) How many microwave photons pass through 1 cm² of this surface each second?

$$\text{Energy per photon } E = hf = h\frac{c}{\lambda} = 1.242$$

$$\text{In } 1 \text{ cm}^2: \text{ Power } P = \frac{NE}{\Delta t} \quad \text{where } N = \# \text{ of photons}$$

$$\therefore N = \frac{P}{E} \Delta t = \frac{(0.01 \text{ J/s})(1 \text{ s})}{1.242 \times 10^{-24} \text{ J}} = 8.0 \times 10^{21} \text{ phot/s}$$


(b) (1 mark) What is the primary physical effect of these photons on human tissue?

Heating, via excitation of rotational motion
of H₂O molecules.

Old MIT exam question

(3)

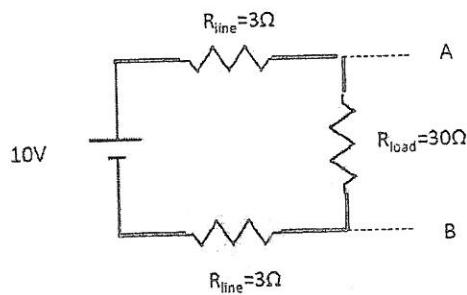9. The circuit below is a simple model of a fictitious town that runs on low voltage DC power. The power is generated by a DC power facility at a voltage of 10V and deliver by two power lines with resistance R_{line} . The maximum power the voltage source can deliver is 5 W.



$$R_{series} = 36 \Omega$$

- (a) (1 mark) Find the total power delivered by the DC voltage source.


$$P = \frac{V^2}{R} = \frac{(10V)^2}{36 \Omega} = 2.78 \text{ W}$$

- (b) (2 marks) Find the power lost to resistance heating in the wires.

$$\begin{aligned} P &= I^2 R_{line} = \left(\frac{V_{source}}{R_{series}} \right)^2 (2 R_{line}) \\ &= \left(\frac{100V}{36 \Omega} \right)^2 (2 \times 3) = 0.463 \text{ W} \end{aligned}$$

($I = 2.78A$)

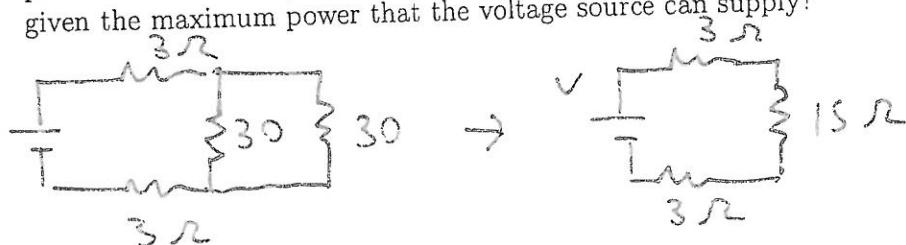- (c) (2 marks) It is proposed that a second town of resistance 30Ω be connected in parallel to the town (across points A and B in the diagram). Will this be possible given the maximum power that the voltage source can supply?



$$P = \frac{V^2}{R_{tot}} = \frac{(10V)^2}{60 \Omega} = 1.67 \text{ W}$$

∴ It is possible

- S -

- (c) (2 marks) Using your knowledge of Faraday's law and magnetic induction briefly explain how this field could cause problems for very sensitive electrical circuits.

A circuit is a closed loop.

A changing field due to AC power lines will induce an emf in the circuit which may affect certain sensitive electric circuits

Old Midterm Question

12. Near the surface of the earth the electric potential V decreases by ≈ 120 V for every meter of elevation increase.

- (a) (1 marks) What is the magnitude and direction of the electric force on a 10 nC charge near the surface of the earth?

Direction: down

Direction of increasing \downarrow $E = -\frac{\Delta V}{\Delta x} \therefore \uparrow E$ points up $\downarrow \vec{F} = q\vec{E}$
 $|F| = (10^{-8} \text{ C})(120 \text{ V}) = 1.2 \times 10^{-6} \text{ N}$ $q < 0$


- (b) (1 marks) Why do humans not observe this voltage in everyday life? (After all, 110V from an outlet can kill)

- Humans are relatively good conductors.
An external electric field cannot induce appreciable internal field in a good conductor (surface charges are set up which oppose any internal field).

- Humans are usually in decent electrical contact w/ the ground. The effect is to deform the lines of constant voltage around the person



7 - 20

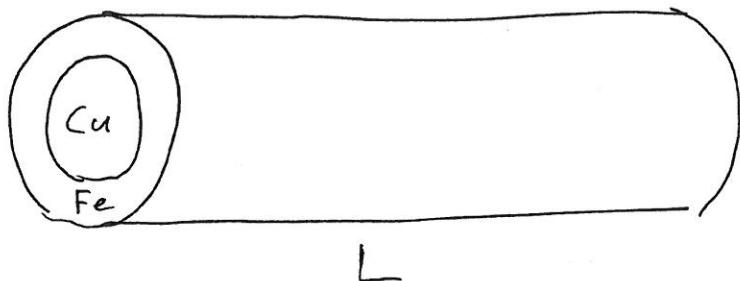

(a)

$$R_{Cu} = \frac{P_{Cu}}{A_{Cu}} L$$


$A_{Cu} + A_{Steel}$ = cross sectional area of copper and iron

$$R_{Fe} = \frac{P_{Fe}}{A_{Steel}} L$$

Resistance of copper core =
 $R_{Cu} = \frac{(1.72 \times 10^{-8} \Omega \text{cm})(10^3 \text{m})}{\pi (0.005 \text{m})^2} = 0.219 \Omega$

$$R_{Fe} = \frac{(29 \times 10^{-8} \Omega \text{cm})(10^3 \text{m})}{\pi (0.01^2 - 0.005^2)} = 1.23 \Omega$$

We add the resistances in parallel!

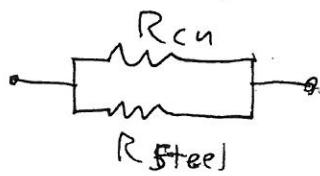

$$\frac{1}{R_{total}} = \frac{1}{R_{Cu}} + \frac{1}{R_{Steel}} = 5.39 \Omega^{-1} \therefore R_{total} = 0.186 \Omega$$

(b) Ratio of currents : Since V is same for each cable

$$I_{Cu} = \frac{V}{R_{Cu}}, I_{Steel} = \frac{V}{R_{Steel}} \quad \frac{I_{Cu}}{I_{Steel}} = \frac{R_{Steel}}{R_{Cu}} = \frac{1.23}{0.219} = \underline{\underline{5.61}}$$

(c) Ratio of powers : $P = V^2/R$

$$\therefore \frac{P_{Cu}}{P_{Steel}} = \frac{R_{Steel}}{R_{Cu}} = \underline{\underline{5.61}}$$

48-16

Q An electric kettle of 7Ω contains 500cm^3 of H_2O at 10°C is connected to 110V supply. If 10% of electrical energy is wasted (bad insulation) how long does it take to convert all water into steam?

- how much energy is required to convert water to steam...

NOTE: $1\text{g H}_2\text{O} = 1\text{cm}^3 \text{H}_2\text{O}$ ($\rho_{\text{H}_2\text{O}} = 1$)

$$\begin{aligned} Q &= mc\Delta T + mL_v \\ &= (.5)(4189)(100-10) + (.5)(2.26 \times 10^6) \\ Q &= 1.3 \times 10^6 \text{ J} \quad (1 \text{ mark}) \end{aligned}$$

- power produced (usable) from kettle

$$P = \frac{(0.9)V^2}{R} = \frac{(0.9)(110)^2}{7} = 1.6 \times 10^3 \text{ W} \quad (1 \text{ mark})$$

- time needed...

$$t = \frac{\text{Joules}}{\text{Joules/s}} = s = \frac{\text{J}}{\text{W}} = \frac{Q}{P}$$

$$\begin{aligned} t &= \frac{1.3 \times 10^6 \text{ J}}{1.6 \times 10^3 \text{ W}} = 8.1 \times 10^2 \text{ s} \\ &\qquad\qquad\qquad = 14 \text{ min} \quad (1 \text{ mark}) \end{aligned}$$

) either is fine


3

46-17


The stove has three settings for its resistors:

- i) in series
- ii) 2 parallel, 1 in series
- iii) all parallel.


Step 1: DIAGRAM

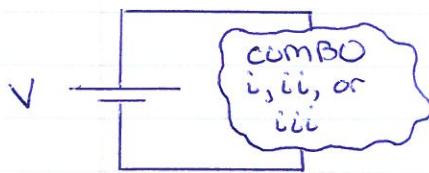

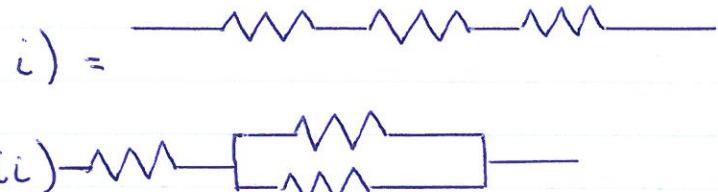- voltage drop across battery is $V_{...}$



iii)

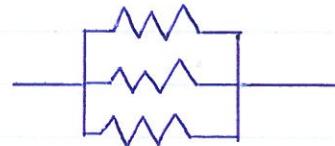

(correct
diagrams
1 mark)

a) which combination gives HIGH, MED, LOW

- refers to heat ~ Power
- total voltage stays the same, but "R" can vary

$$P = \frac{V^2}{R} \quad \therefore \text{low } R \rightarrow \text{high } P$$
$$\text{big } R \rightarrow \text{low } P$$

HIGH	is	(iii)
MED	is	(ii)
LOW	is	(i)

(1 mark)

b) what is R_{TOTAL} for each case?

i) $R_{\text{TOTAL}} = 3R$

(1 mark)

ii) $R_{\text{TOTAL}} = \left(\frac{1}{R}\right)^{-1} + R = \frac{3R}{2}$

iii) $R_{\text{TOTAL}} = \left(\frac{1}{R} + \frac{1}{R} + \frac{1}{R}\right)^{-1} = \left(\frac{3}{R}\right)^{-1} = \frac{R}{3}$

c) if HIGH setting provides 1000 W, what is the power of the other two?

- use P_{HIGH} to get "R" for each resistor...

$$P_{HIGH} = \frac{V_{TOTAL}^2}{R_{TOTAL}} = 1000 \text{ W}$$

NOTE: if R_{TOTAL} increases by factor of "A", the power decreases by factor of " $1/A$ ".

- the $R_{TOTAL(HIGH)}$ is $R/3$

- $R_{TOTAL(MED)} = 3R/2$

- increased by $\frac{3R}{2}/\frac{R}{3} = \frac{9}{2}$

- $\boxed{\text{Power (MED)}} = 1000 \cdot \frac{2}{9} = \boxed{222 \text{ W}}$ (1 mark)

- $R_{TOTAL(LOW)} = 3R$

- increased by $\frac{3R}{R/3} = 9$

- $\boxed{\text{Power (LOW)}} = 1000 \cdot \frac{1}{9} = \boxed{111 \text{ W}}$ (1 mark)

- not really a good set of values, linear scale is preferred.