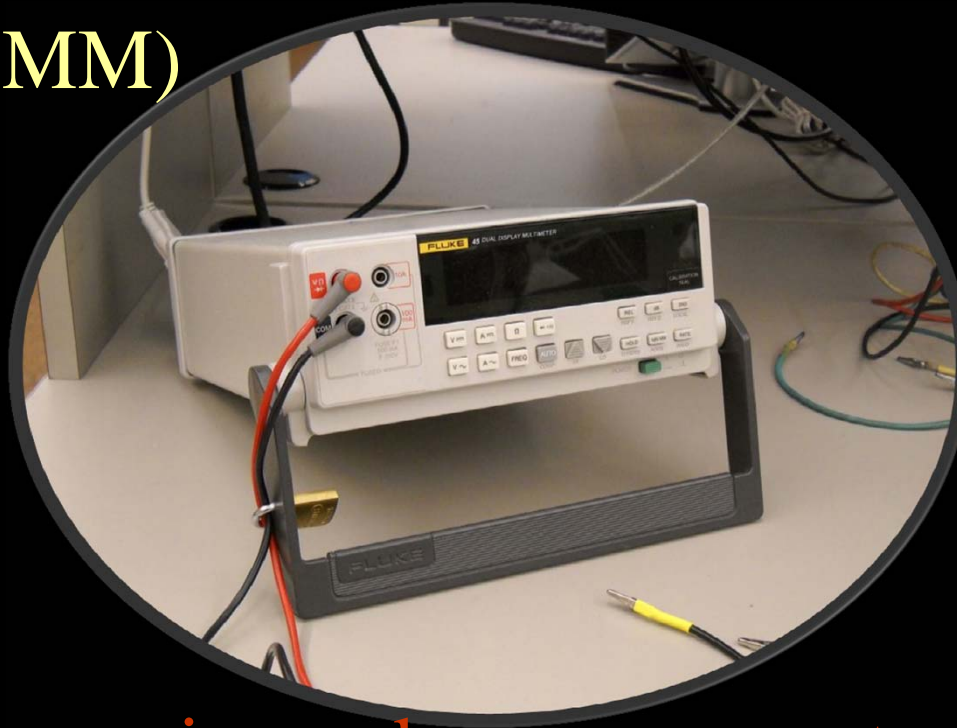


Digital Multi Meter (DMM)



DC & AC Voltage

Ohms (Resistance)

DC & AC Current

100mA & 10A

Range



(Move the red-terminal)

For measuring unknown current,
always use 10A socket first



If the measured current is less than 100mA
then move the red terminal to the 100mA range

100mA Fuse

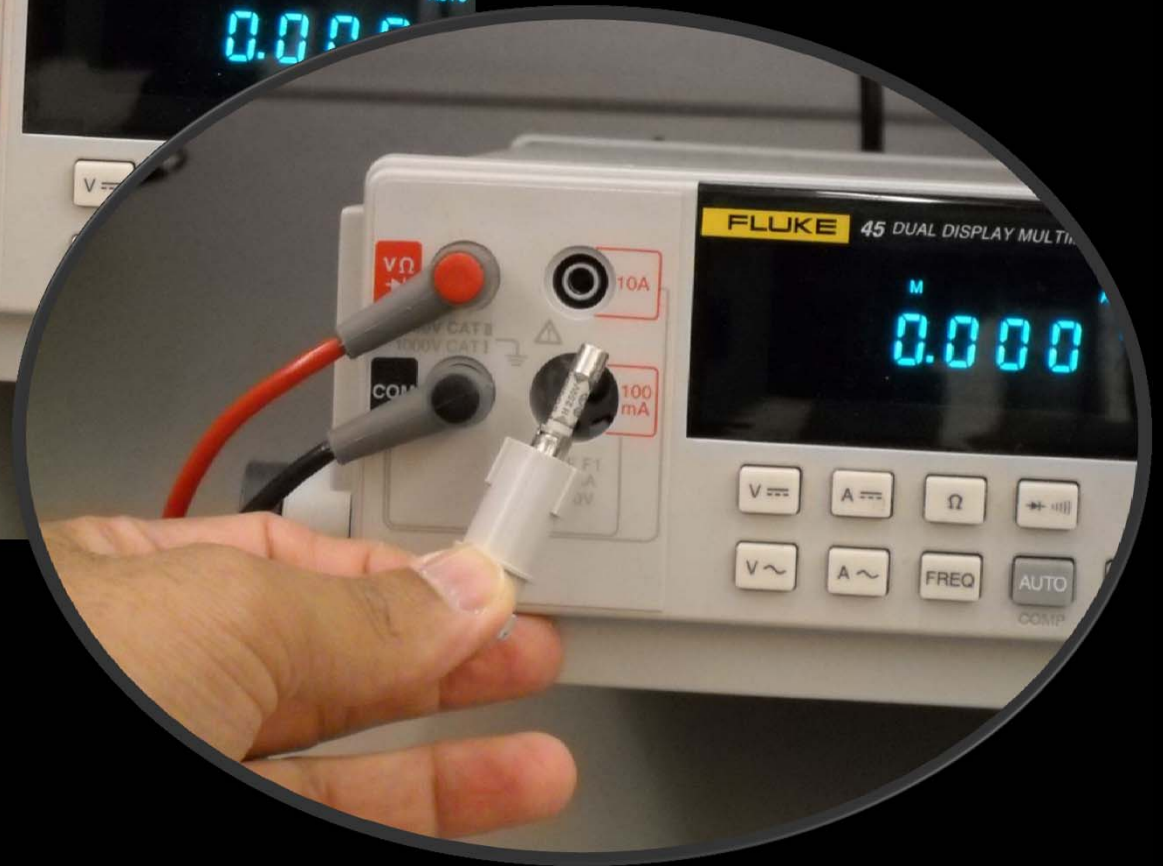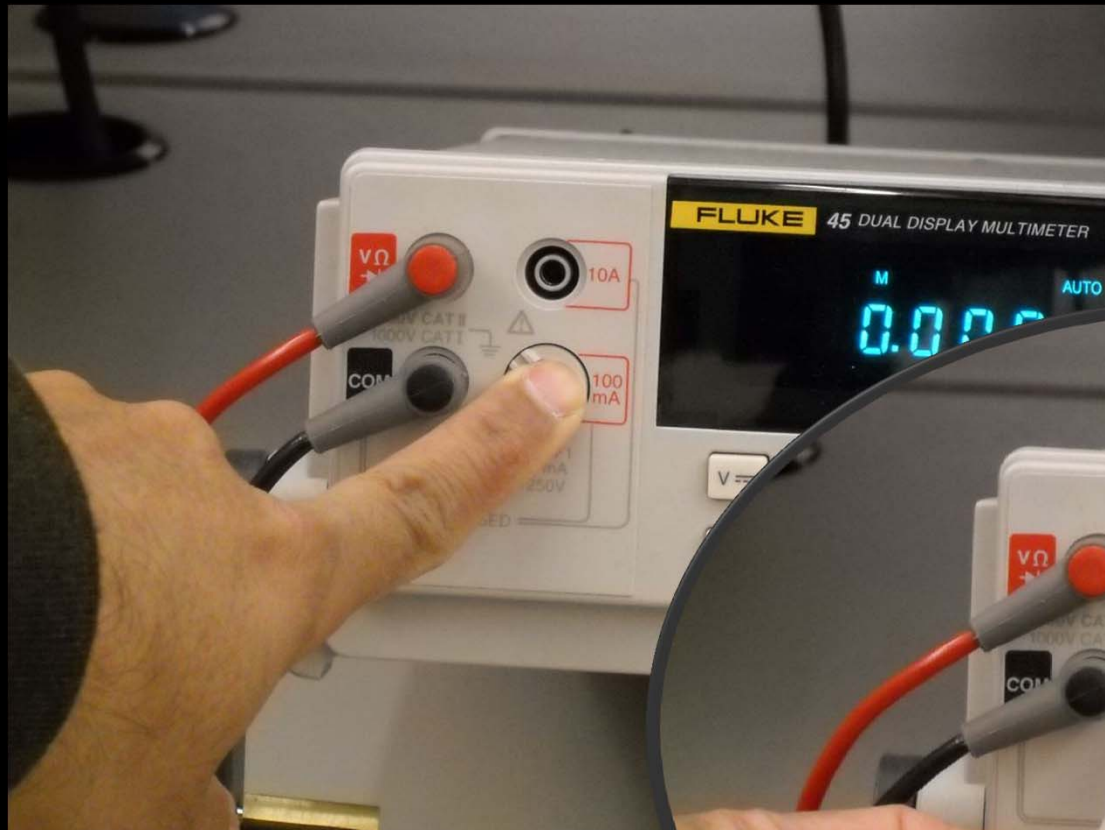

All modern digital meters are basically
a voltage measurement device

Accuracy of DMM


Voltage $\pm (0.02\% + 2 \text{ Digit})$

Current $\pm (0.05\% + 3 \text{ Digit})$

Resistance $\pm (0.05\% + 2 \text{ Digit})$

When you make any measurement notice
how many decimal places the display show

A measurement exercise

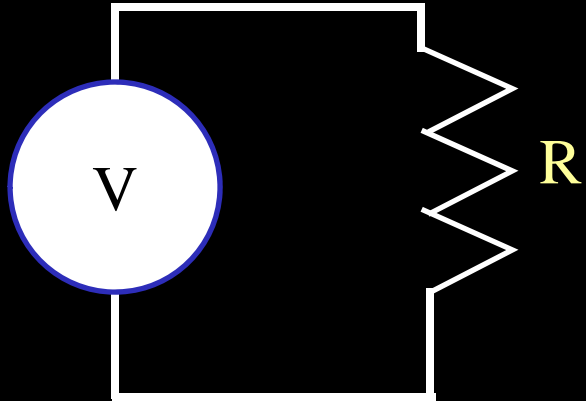

Verify Ohm's law experimentally

Show your measurement and calculation reconciles within the instrument accuracy

Picked a 470 Ω resistor
from the bin

Measured the value
using DMM

Measured the voltage
applied using DMM


Measured the current
using DMM

$$0.499\text{V} \div 468\Omega = 1.066\text{mA}$$

Then why does the meter
read 1.04mA?

2% error!

Meter specification:
0.05% + 2 Digit

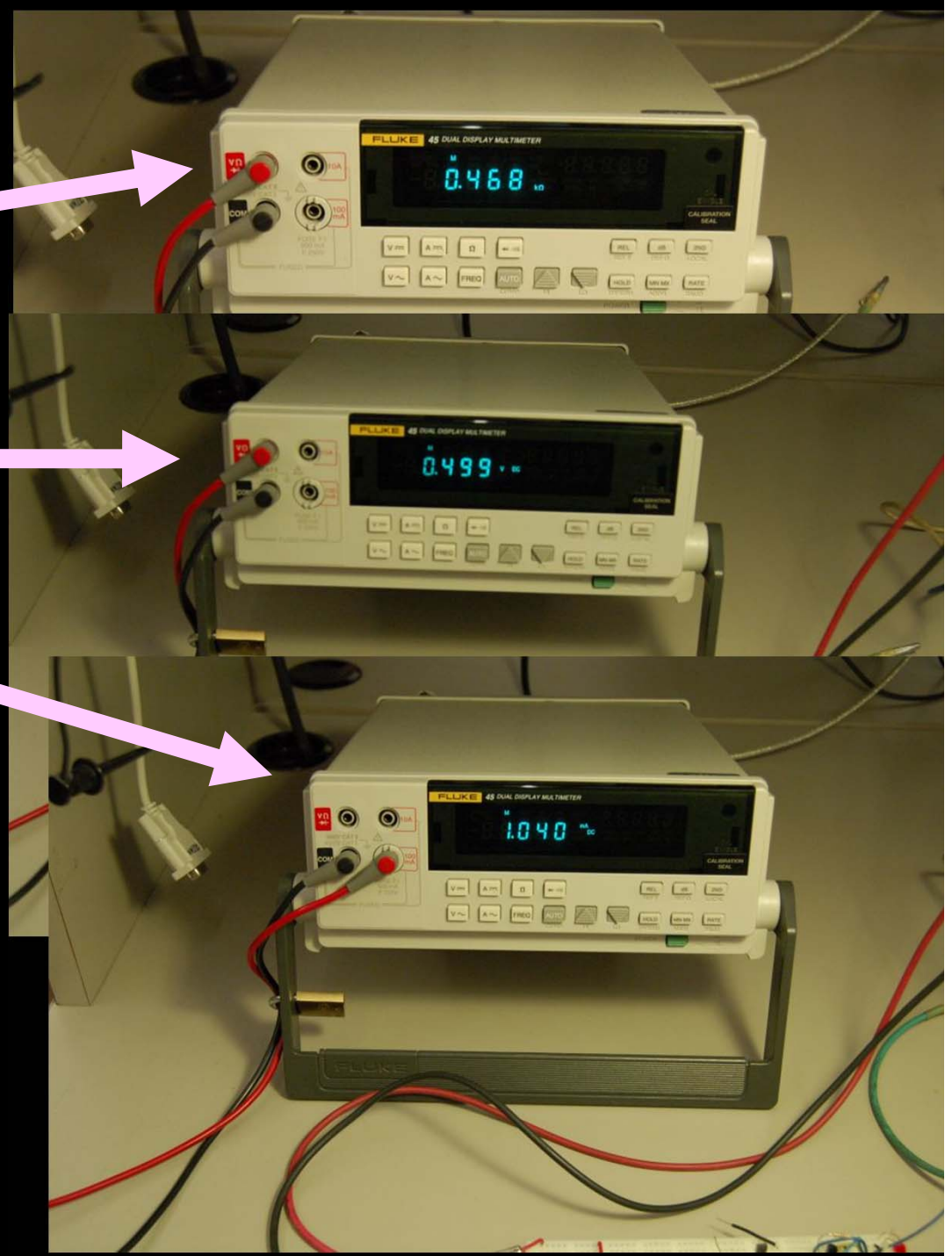


During current measurement a resistor is introduced in series
(Shunt Resistor or meter burden)

We have to include this in our calculation

100mA range: 11.5Ω 10A range: 0.5Ω


Lets take into account the accuracy of our measurements

Resistance measurement:

$$0.468 \pm (0.05\% + 2 \text{ Digit}) \quad 0.468 \pm \left[0.468 \times \left(\frac{0.05}{100} \right) + (2 \times 0.001) \right]$$



470.234Ω
 465.766Ω

Voltage measurement:

$$0.499 \pm (0.02\% + 2 \text{ Digit}) \quad 0.499 \pm \left[0.499 \times \left(\frac{0.02}{100} \right) + (2 \times 0.001) \right]$$


0.5011V
 0.4969V

Current measurement:

$$1.04 \pm (0.05\% + 3 \text{ Digit}) \quad 1.04 \pm \left[1.04 \times \left(\frac{0.05}{100} \right) + (3 \times 0.001) \right]$$


1.04352mA
 1.03648mA

Re-Calculate the current including the shunt resistance

470.234Ω

Max possible current

$$\frac{0.5011}{465.766 + 11.5} = 1.0499mA$$

465.766Ω

Min possible current

$$\frac{0.4969}{470.234 + 11.5} = 1.0314mA$$

0.5011V

0.4969V

1.04352mA

1.0499mA

1.040mA

1.04065mA

0.06%

1.03648mA

1.0314mA

Measured

Calculated