

$$V_i - 10^3 i_1 - 10^3 i_2 = 0$$

$$V_o - 3 \times 10^3 i_2 - 10^3 i_2 = 0$$

$$V_i - 10^3 i_1 - 2 \times 10^3 i_1 - V_o = 0$$

Hence,

$$10^3 i_1 + 10^3 i_2 = V_i$$

$$4 \times 10^3 i_2 = V_o$$

$$3 \times 10^3 i_2 + V_o = V_i$$

Since $i_2 = \frac{V_o}{4 \times 10^3}$, then


$$i_1 + i_2 = \frac{V_i}{10^3}$$

$$3 \times 10^3 \cdot i_1 + V_o = V_i \Rightarrow i_1 = \frac{V_i - V_o}{3 \times 10^3}$$

$$\frac{V_i - V_o}{3 \times 10^3} + \frac{V_o}{4 \times 10^3} = \frac{V_i}{10^3} \quad / 12 \times 10^3$$


$$4V_i - 4V_o + 3V_o = 12V_i \quad \text{or:} \quad \frac{V_o}{V_i} = -8$$

2

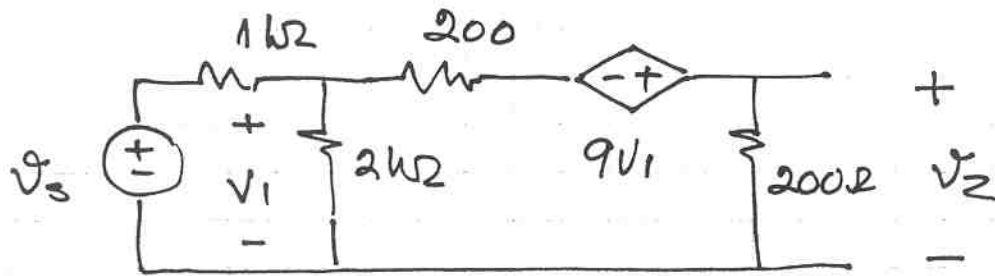

2

Source transformation: 200Ω

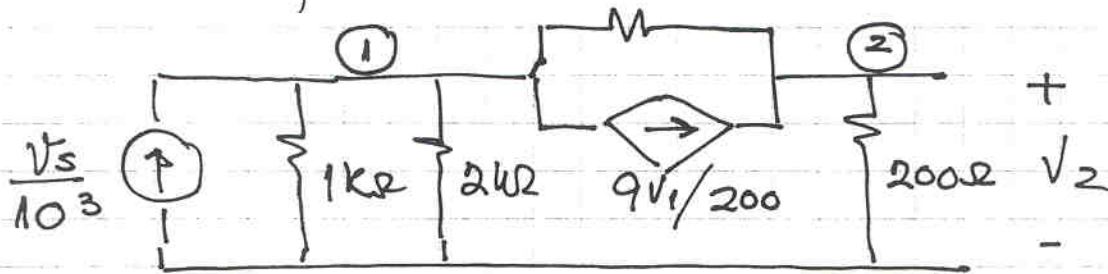

Nodal equation:

$$\frac{v_1}{10^3} + \frac{v_1}{2 \times 10^3} + \frac{v_1 - v_2}{200} + \frac{9v_1}{200} = \frac{v_s}{10^3} \times 2 \times 10^3$$

$$\frac{v_2}{200} + \frac{v_2 - v_1}{200} - \frac{9v_1}{200} = 0$$

Hence, $3v_1 + 10(v_1 - v_2) + 90v_1 = 2v_s$

$$2v_2 - 10v_1 = 0$$

or: $103v_1 - 10v_2 = 2v_s$

$$v_2 = 5v_1$$

$$i = \frac{10^{-3} \cdot v_x}{6 + \frac{1}{5} + \frac{2}{3}}$$

$$i = \frac{15}{103} \times 10^{-3} \cdot v_x$$

Then, $v_x = \frac{v_x}{200} + i$

$$v_x = \frac{v_x}{200} + \frac{15}{103} \times 10^{-3} \cdot v_x$$

$$\frac{v_x}{i} = \frac{1}{\frac{1}{200} + \frac{15}{103} \times 10^{-3}}$$

$$R_{Th} = \frac{v_x}{i_x}$$

$$R_{Th} = \frac{10^3}{5 + \frac{15}{103}}$$

$$R_{Th} = \frac{103}{530} \times 10^3 \Omega$$



$$R_{Th} = \frac{103}{530} k\Omega$$

$$103V_1 - 50V_1 = 2Vs$$

$$V_1 = \frac{2}{53}Vs$$

Therefore equivalent resistance:
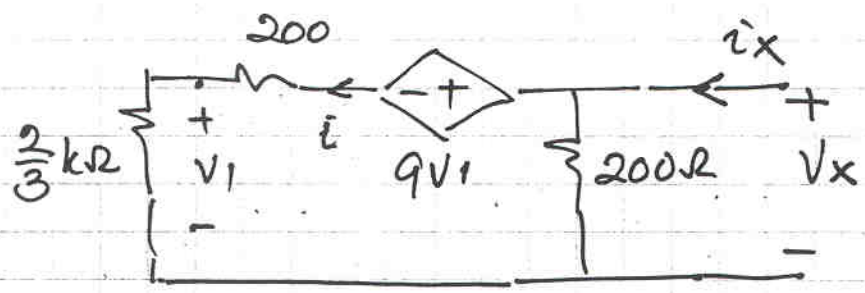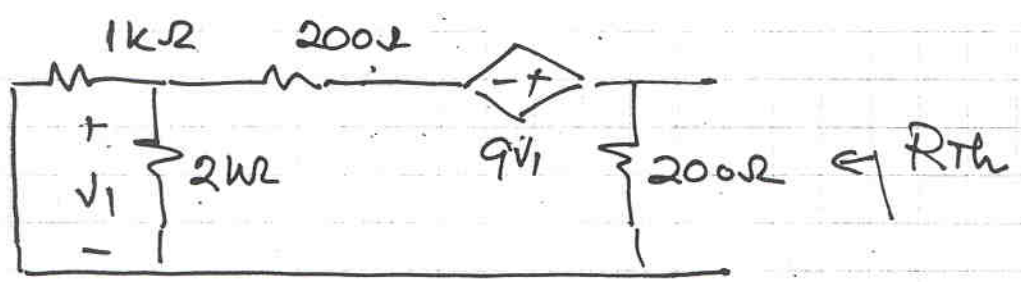
$$Vs \equiv 0 ; \text{ or } i_s \equiv 0$$





$$\text{Hence, } V_x - 9V_1 - 200i - \frac{2}{3} \times 10^3 \cdot i = 0$$

$$V_1 = \frac{2}{3} \times 10^3 \cdot i$$

$$V_x = 9 \cdot \frac{2}{3} \times 10^3 i + 200i + \frac{2}{3} \times 10^3 i$$


$$i = \frac{V_x}{6 \times 10^3 + 200 + \frac{2}{3} \times 10^3}$$

⑧

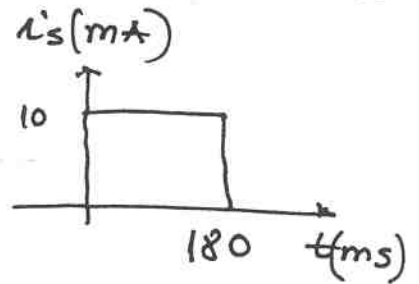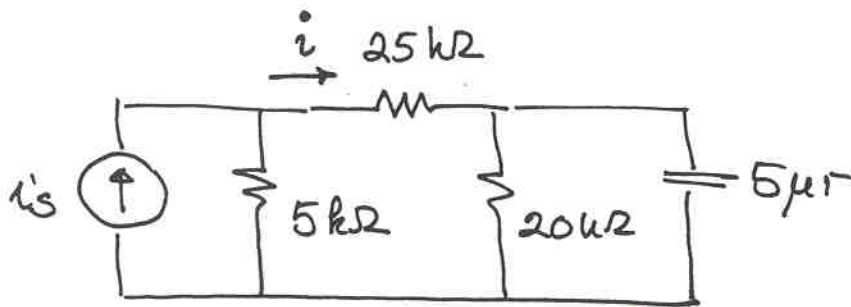

for $t < 0$ $i_s(t) = 0$

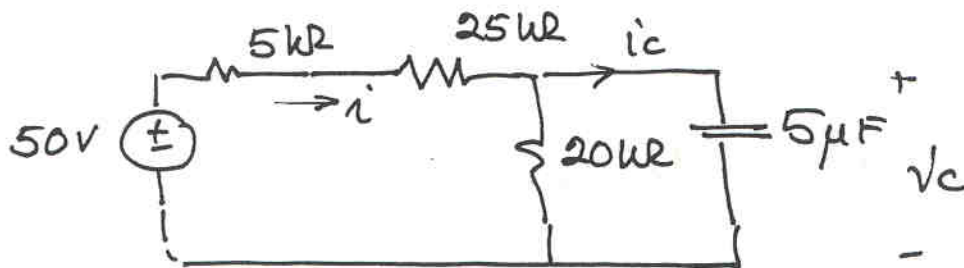for $0 < t < 180 \text{ ms}$; $i_s = 10 \text{ mA}$



$$50 - 30 \times 10^3 \cdot i' - v_c = 0$$

$$v_c = 5 \times 10^{-6} \cdot \frac{dv_c}{dt}$$

$$i' = i_c + \frac{v_c}{20 \times 10^3}$$

$$30 \times 10^3 \cdot i' + v_c = 50$$

$$i' = 5 \times 10^{-6} \cdot \frac{dv_c}{dt} + \frac{v_c}{20 \times 10^3}$$

Here, state equation is:

$$30 \times 10^3 \cdot \left(5 \times 10^{-6} \cdot \frac{dv_c}{dt} + \frac{v_c}{20 \times 10^3} \right) + v_c = 50$$

$$30 \times 10^3 \cdot \left(5 \times 10^{-6} \cdot \frac{dV_c}{dt} + \frac{V_c}{20 \times 10^3} \right) + V_c = 50$$

$$150 \times 10^{-3} \cdot \frac{dV_c}{dt} + \frac{3}{2} V_c + V_c = 50$$

$$\frac{dV_c}{dt} + \frac{5}{300 \times 10^{-3}} V_c = \frac{50}{150 \times 10^{-3}}$$

$$\frac{dV_c}{dt} + \frac{10^3}{60} V_c = \frac{10^3}{3}$$

Natural frequency: $s = -\frac{10^3}{60}$; $s = -\frac{50}{3}$

$$V_c(t) = V_{c_h}(t) + V_{c_p}(t)$$

$$V_{c_h}(t) = K_1 e^{-\frac{10^3}{60}t}$$

$$V_{c_p}(t) = A ; \frac{10^3}{60} \cdot A = \frac{10^3}{3} ; A = 20$$

$$V_c(t) = K_1 e^{-\frac{10^3}{60}t} + 20$$

$$V_c(0^-) = 0 ; V_c(0^+) = 0 \Rightarrow K_1 + 20 = 0 ; K_1 = -20$$

$$V_c(t) = 20 (1 - e^{-\frac{10}{3}t})$$

$$\Delta t \ t = 180 \text{ms} : V_c(180 \text{ms}) = 20 (1 - e^{-\frac{10}{3} \times 180 \times 10^{-3}})$$

$$V_c(180 \text{ms}) = 20 \cdot (1 - e^{-3})$$

Since $e^{-3} = 0.05$ $V_c(180 \text{ms}) = 20 (1 - 0.05)$

$$V_c(180 \text{ms}) = 19 \text{V}$$

For $t > 180 \text{ ms}$

$$\frac{dV_c}{dt} + \frac{10^3}{60} \cdot V_c = 0$$

< The same LHS as before >

$$V_c(t) = k_2 e^{-\frac{10^3}{60} \cdot t}$$

$$V_c(t) = k_2 e^{-\frac{50}{3}t}$$

$$\begin{aligned} V_c(180^+ \text{ms}) &= k_2 e^{-\frac{50}{3} \times 180 \times 10^{-3}} \\ &= k_2 e^{-3} \end{aligned}$$

$$V_c(180^+ \text{ms}) = V_c(180^- \text{ms})$$

Hence, $k_2 e^{-3} = 20(1 - e^{-3})$

$$k_2 = 20(e^3 - 1) \quad \text{or} \quad k_2 = 20 \cdot (19 - 1)$$

$$k_2 = 380$$

And $V_c(t) = 20(e^3 - 1)e^{-\frac{50}{3}t}$

or

$$V_c(t) = 380 e^{-\frac{50}{3}t}$$

For $t < 180 \text{ ms}$:

$$\text{Current } i(t) = C \frac{dv_c}{dt} + \frac{v_c}{20 \times 10^3}$$

$$i(t) = 5 \times 10^{-6} \cdot \frac{dv_c}{dt} + \frac{v_c}{20 \times 10^3}$$

Recall that

$$v_c(t) = 20(1 - e^{-\frac{10}{3}t})$$

$$i(t) = 5 \times 10^{-6} \cdot 20 \cdot \frac{10}{3} e^{-\frac{10}{3}t} + \frac{20 \cdot (1 - e^{-\frac{10}{3}t})}{20 \times 10^3}$$

$$i(t) = \frac{5}{3} \times 10^{-3} \times e^{-\frac{10}{3}t} + 1 \times 10^{-3} - 1 \times 10^{-3} \times e^{-\frac{10}{3}t}$$

$$i(t) = (1 + \frac{2}{3} e^{-\frac{10}{3}t}) \times 10^{-3}$$

$$\text{For } t > 180 \text{ ms} \quad v_c(t) = 20(e^3 - 1)e^{-\frac{10}{3}t}$$

$$i(t) = C \frac{dv_c}{dt} + \frac{v_c}{20 \times 10^3}$$

$$i(t) = 5 \times 10^{-6} \times 20(e^3 - 1) \cdot \left(-\frac{10}{3} e^{-\frac{10}{3}t}\right) + \frac{20(e^3 - 1)e^{-\frac{10}{3}t}}{20 \times 10^3}$$

$$i(t) = -\frac{5}{3} \times 10^{-3} \times (e^3 - 1) e^{-\frac{10}{3}t} + 10^{-3} (e^3 - 1) e^{-\frac{10}{3}t}$$

$$i(t) = -\frac{2}{3} (e^3 - 1) e^{-\frac{10}{3}t}$$

$$\text{Let } e^3 = 20$$

$$i(t) = -\frac{38}{3} e^{-\frac{10}{3}t}$$

Note that:

$$e'(0) = 10^{-3} \cdot \left(1 + \frac{2}{3}\right) \quad ; \quad e'(0) = \frac{5}{3} \times 10^{-3} \text{ A}$$

$$i(0) = \frac{5}{3} \text{ mA}$$

$$e'(180 \text{ ms}^-) = \left(1 + \frac{2}{3} \cdot e^{-\frac{10}{3} \times 180 \times 10^{-3}}\right) \times 10^{-3}$$

$$= \left(1 + \frac{2}{3} \cdot e^{-3}\right) \times 10^{-3}$$

Let $e^{-3} = 0.05$

$$e'(180 \text{ ms}^-) = \left(1 + \frac{2}{3} \times 0.05\right) \times 10^{-3}$$

$$= \frac{31}{30} \text{ mA}$$

$$e'(180 \text{ ms}^+) = -\frac{2}{3} (e^3 - 1) \times e^{-\frac{10}{3} \times 180 \times 10^{-3}}$$


$$= -\frac{2}{3} \cdot (e^3 - 1) \cdot e^{-3}$$

$$= -\frac{2}{3} (1 - e^{-3})$$

$$= -\frac{2}{3} (1 - 0.05)$$


$$= -\frac{19}{30} \text{ mA}$$

Note:
 $i(\infty) \rightarrow 0$

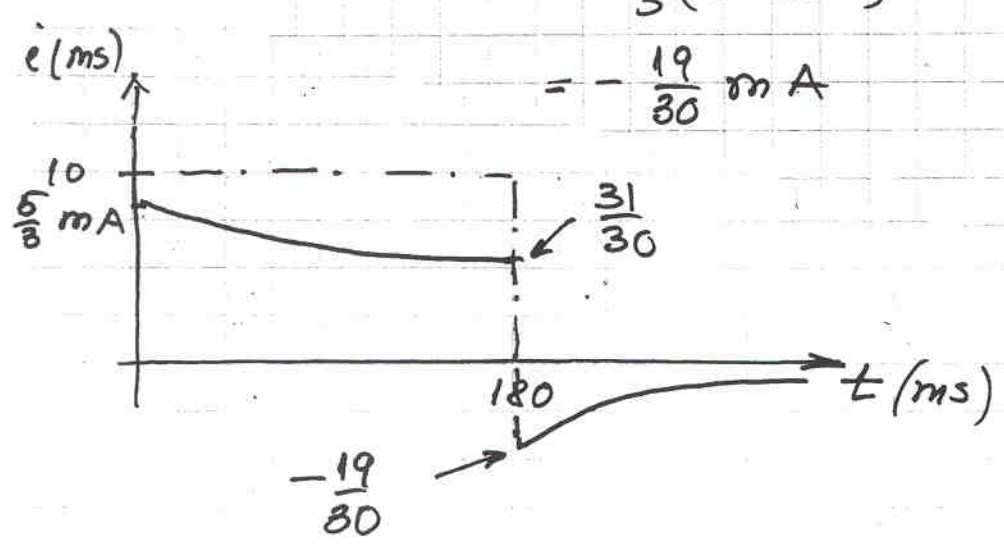

4

10u(t)

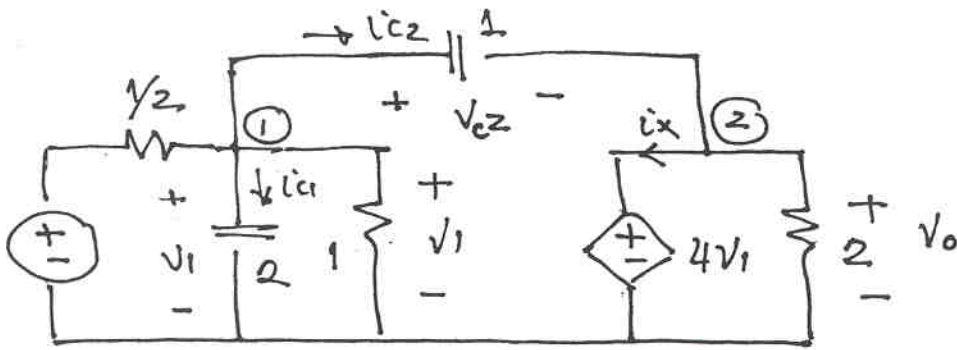

$$\textcircled{1} \quad \frac{v_1 - 10}{1/2} + 1i_{c1} + 1i_{c2} + \frac{v_1}{1} = 0$$

$$\textcircled{2} \quad v_2 = 4v_1$$

$$\textcircled{2} \quad -1i_{c2} + i_x + \frac{v_2}{2} = 0$$

$$2(v_1 - 10) + 1i_{c1} + 1i_{c2} + v_1 = 0$$

$$v_2 = 4v_1$$

$$i_{c1} = 2 \frac{dv_1}{dt}$$

$$i_{c2} = \frac{d(v_1 - v_2)}{dt}$$

$$3v_1 + 2 \frac{dv_1}{dt} + \frac{d}{dt}(v_1 - v_2) = 20$$

$$3 \frac{dv_1}{dt} - \frac{dv_2}{dt} + 3v_1 = 20$$

$$v_2 = 4v_1$$

$$- \frac{dv_1}{dt} + 3v_1 = 20$$

$$- \frac{dv_1}{dt} + 3v_1 = 20$$

$$-s + 3 = 0 \quad \underline{\underline{s = 3}}$$

$$V_1 = Ke^{3t} + A$$

$$V_{1p} = A \quad ; \quad 3A = 20$$

$$A = \frac{20}{3}$$

$$V_2(0) = 0$$

$$k + A = 0 \quad ; \quad k = -\frac{20}{3}$$

$$V_1 = \frac{20}{3} (1 - e^{3t}) \quad ; \quad V_{c1} = \frac{20}{3} (1 - e^{3t})$$

$$V_2 = 4 \cdot \frac{20}{3} (1 - e^{3t}) \quad ; \quad V_{c2} = -20 (1 - e^{3t})$$

$$V_2 = \frac{80}{3} (1 - e^{3t})$$


$$V_{c2} = V_2 - V_1$$

It is a first order circuit.

$$V_o = 4V_1$$

$$V_o = V_2 \quad ; \quad V_o = \frac{80}{3} (1 - e^{3t})$$

5

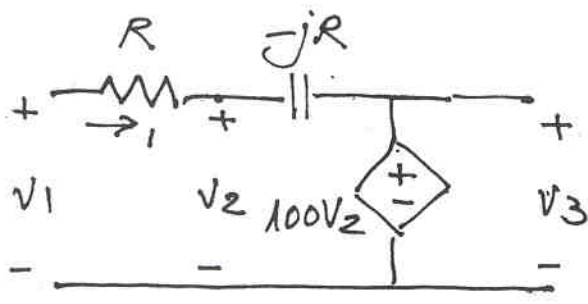

$$V_1 - R \cdot i + jR \cdot i - 100 \cdot V_2 = 0$$

$$V_3 = 100 \cdot V_2$$

$$V_1 - R \cdot i - V_2 = 0 ; V_2 = V_1 - R \cdot i$$

$$\text{or: } i = \frac{V_1 - V_2}{R}$$

$$V_1 - R(1-j) \cdot \frac{V_1 - V_2}{R} - 100V_2 = 0$$

$$V_1 - (1-j)(V_1 - V_2) - 100V_2 = 0$$

$$V_1 - (1-j)V_1 + (1-j)V_2 - 100V_2 = 0$$

$$j \cdot V_1 - (99+j) \cdot V_2 = 0$$

$$V_2 = \frac{j}{99+j} V_1$$

$$\underline{V_3} = \frac{100j}{99+j} \underline{V_1}$$

$$\underline{V_3} = \frac{100}{\sqrt{99^2+1}} \cdot \frac{e^{j\pi/2}}{e^{j\arctan(1/99)}} \cdot \underline{V_1}$$

$$\text{or } \underline{V_3} = \frac{100}{1-99j} \cdot \underline{V_1}$$

$$\underline{V_3} = \frac{100}{\sqrt{99^2+1}} \cdot e^{j\arctan(99)} \underline{V_1}$$

$$\underline{A} = \frac{100}{\sqrt{99^2+1}} \cdot e^{j(\frac{\pi}{2} - \text{arctg } 1/99)}$$

$$|A| = \frac{100}{\sqrt{99^2+1}} \quad |A| \approx 1$$

$$\text{arg } \underline{A} = \frac{\pi}{2} - \text{arctg } 1/99 \quad \text{arg } \underline{A} \approx \pi/2$$