

SIMON FRASER UNIVERSITY  
SCHOOL OF ENGINEERING SCIENCE

Fall 2008  
ENSC 220: ELECTRIC CIRCUITS I

Final Examination  
Wednesday, December 10, 2008

*Duration: 3 hours. Attempt all problems. Questions are not equally weighted. Closed book and closed notes. Simple calculators (with no graphing/programming functions) are permitted. Formula/equation sheets, PDAs, laptops, and wireless phones are not permitted.*

1. A model of one-transistor amplifier circuit is shown in Figure 1. The transistor is modeled with the circuit connected between terminals B-C-E. Find the Thévenin's equivalent seen between the base (B) and the emitter (E) terminals using the following procedure:  
(20 points) The Thévenin's equivalent voltage:
  - Write **nodal equations** for an **appropriate circuit**.
  - Find the Thévenin's equivalent voltage  $V_{Th}$ .(20 points) The Thévenin's equivalent resistance:
  - Write **mesh equations** for an **appropriate circuit**.
  - Find the Thévenin's equivalent resistance  $R_{Th}$ .
  - Check your result by observing the resulting circuit when  $\beta = 0$ .
2. (20 points) The capacitor shown in Figure 2 is initially uncharged. Suppose that  $v_s(t) = 2tu(t)$  (a ramp function).
  - Find capacitor voltage  $v_c(t)$  for  $t \geq 0$ .
  - Find current  $i(t)$  for  $t \geq 0$ .
  - Sketch  $v_c(t)$  and  $i(t)$  as functions of time.
3. (20 points) In the circuit shown in Figure 3, the switch  $S$  has been at position  $A$  for a long time and is moved to position  $B$  at  $t = 0$ .
  - Find  $v_C(0-)$  and  $i_L(0-)$ .
  - Find  $v_C(t)$  for  $t \geq 0$ .
  - Find  $v_C(t)$  and  $i_L(t)$  for  $t \rightarrow \infty$ .
4. (20 points) The ideal op amp circuits shown in Figure 4 operates in the sinusoidal steady-state with an input voltage  $v_i(t) = V_m \cos(\omega t)$ .
  - Find the phasor of the output voltage  $V_o$ .
  - Find the ratio  $V_o/V_i$ .
  - Find frequency  $\omega$  as a function of  $L$  and  $C$  so that the ratio does not depend of  $\omega$ .
  - For this value of  $\omega$  write the relationship between  $v_o(t)$  and  $v_i(t)$ .

Fig. 1.

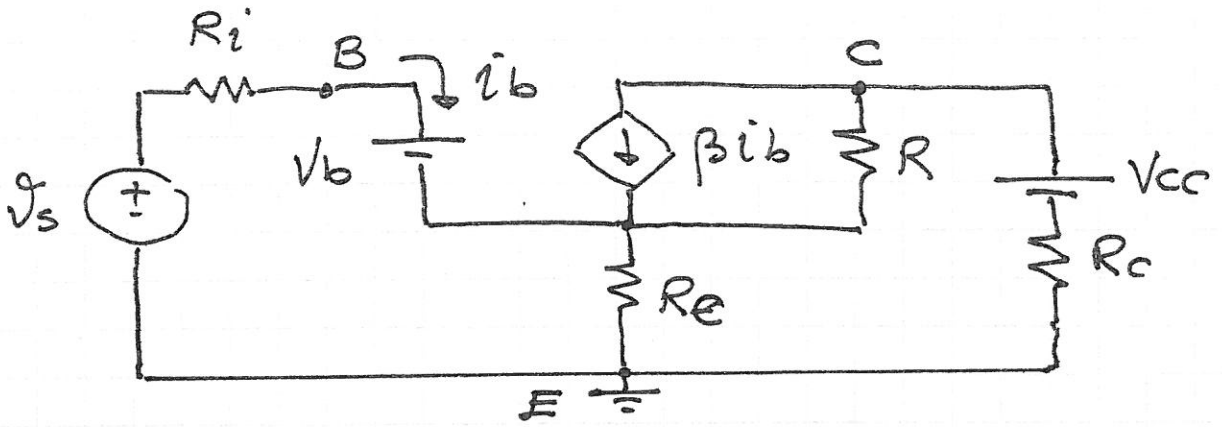


Fig. 2.

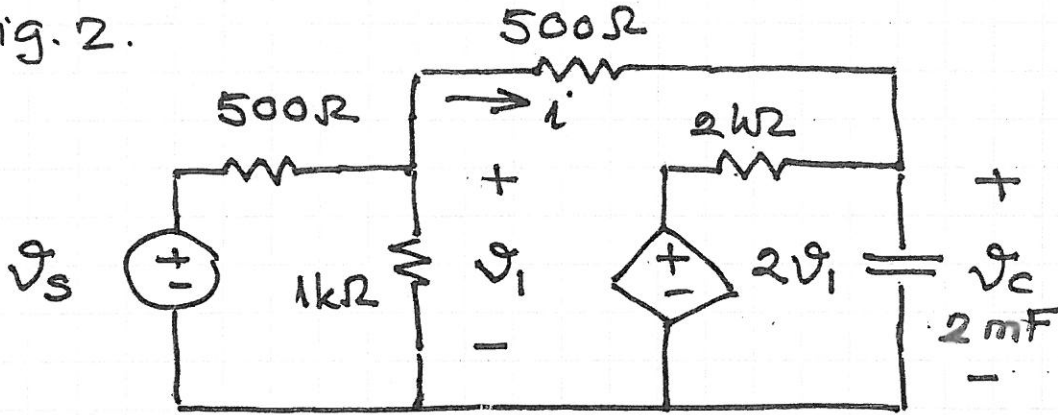


Fig. 3.

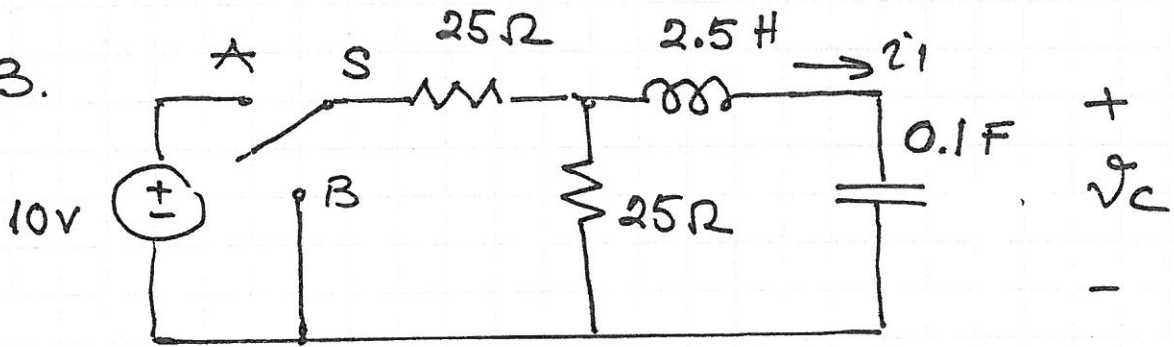


Fig. 4.

