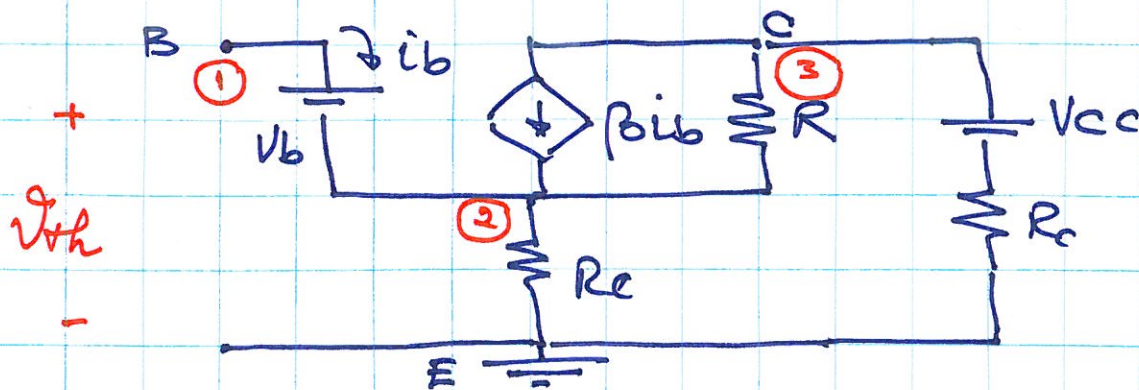


Thevenin voltage:

Nodal equations should be written for the circuit.



Nodes B and E are open-circuited.

Hence: $i_b = 0$

Nodal equations:

$$V_1 - V_2 = V_b$$

$$\frac{V_2}{R_e} - \beta \cdot i_b + \frac{V_2 - V_3}{R} = 0$$

$$\beta i_b + \frac{V_3 - V_2}{R} + \frac{V_3 - V_{cc}}{R_c} = 0$$

Since $i_b = 0$:

$$V_1 - V_2 = V_b$$

(2)

$$V_2 \left(\frac{1}{R_e} + \frac{1}{R} \right) - V_3 \cdot \frac{1}{R} = 0 \quad (1)$$

$$-\frac{1}{R} \cdot V_2 + V_3 \cdot \left(\frac{1}{R_c} + \frac{1}{R} \right) = \frac{V_{CC}}{R_c} \quad (2)$$

Thevenin voltage: $V_{Th} = V_1$; It suffices to find V_2
From the 1st equation: Since $V_1 = V_2 + V_b$

$$V_3 = R \cdot \left(\frac{1}{R_e} + \frac{1}{R} \right) V_2$$

Substituting into (2) leads to:

$$-\frac{1}{R} \cdot V_2 + R \cdot \left(\frac{1}{R_e} + \frac{1}{R} \right) \cdot \left(\frac{1}{R_c} + \frac{1}{R} \right) V_2 = \frac{V_{CC}}{R_c}$$

Hence,

$$V_2 = \frac{V_{CC}}{R_c} \cdot \frac{1}{-\frac{1}{R} + \frac{R}{R_e} \cdot \left(\frac{1}{R_c} + \frac{1}{R} \right) + \frac{1}{R_c} + \frac{1}{R}}$$

$$V_2 = \frac{V_{CC}}{R_c} \cdot \frac{1}{\frac{R}{R_c \cdot R_c} + \frac{1}{R_c} + \frac{1}{R_c}}$$

$$V_2 = \frac{V_{CC} \cdot R_c}{R + R_e + R_c}$$


Finally:

$$V_{Th} = V_1$$

$$V_{Th} = V_2 + V_b$$

$$V_{Th} = V_b + V_{CC} \cdot \frac{R_c}{R + R_e + R_c}$$

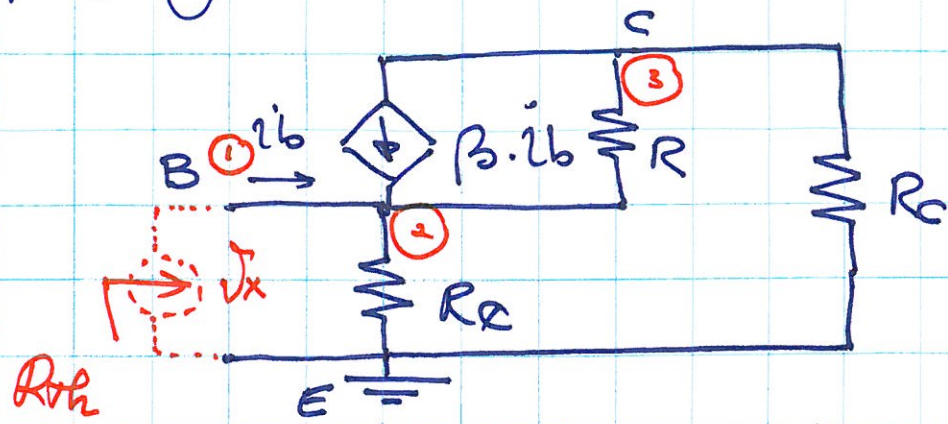
To find Thevenin resistance, we consider the same circuit but with independent sources properly disconnected:




Assume a voltage source v_x is connected between terminals B and E. Then:

$$R_{th} = \frac{v_x}{i_b}$$

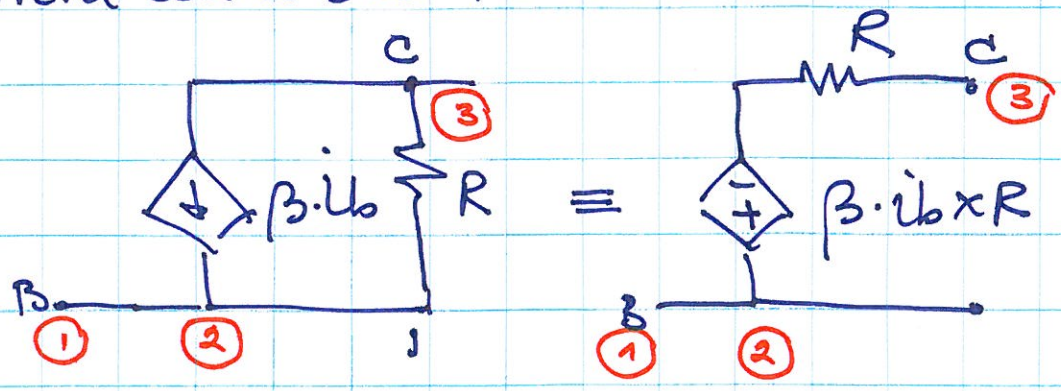Transform the parallel connection of the dependent current source and the resistor.



The equivalent circuit is:

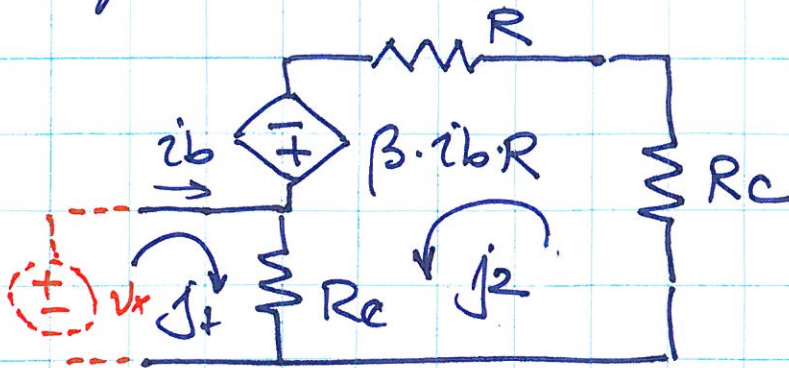

Mesh equations:

$$v_x - R_e(j_1 + j_2) = 0$$

$$\beta \cdot i_b \cdot R - R_e(j_1 + j_2) - (R + R_c) \cdot j_2 = 0$$

Note that $i_b = j_1$

Hence:

$$R_e \cdot j_1 + R_e \cdot j_2 = v_x$$

$$-(R_e - \beta \cdot R) \cdot j_1 - (R + R_e + R_c) \cdot j_2 = 0$$

Since $R_{th} = \frac{v_x}{j_1}$, let us find j_2 in terms of j_1 :

$$j_2 = -j_1 + \frac{v_x}{R_e}$$

From the second equation:

$$-(R_e - \beta R) \cdot j_1 - (R + R_e + R_c) \cdot \left(-j_1 + \frac{v_x}{R_e}\right) = 0$$

$$j_i(\beta R + R + R_c) = \frac{R + R_e + R_c}{R_c} \cdot V_x$$

Hence: $R_{th} = \frac{V_x}{j_i}$

$$R_{th} = \frac{R_c \cdot (\beta R + R + R_c)}{R + R_e + R_c}$$

or $R_{th} = R_c \cdot \frac{(1 + \beta)R + R_c}{R + R_e + R_c}$


Check:

If $\beta \rightarrow 0$ $R_{th} = R_c \cdot \frac{R + R_c}{R + R_e + R_c}$


From the circuit: R_a and R_c are connected in series and then in parallel with R_e

If $\beta \rightarrow \infty$ $R_{th} = R_e$

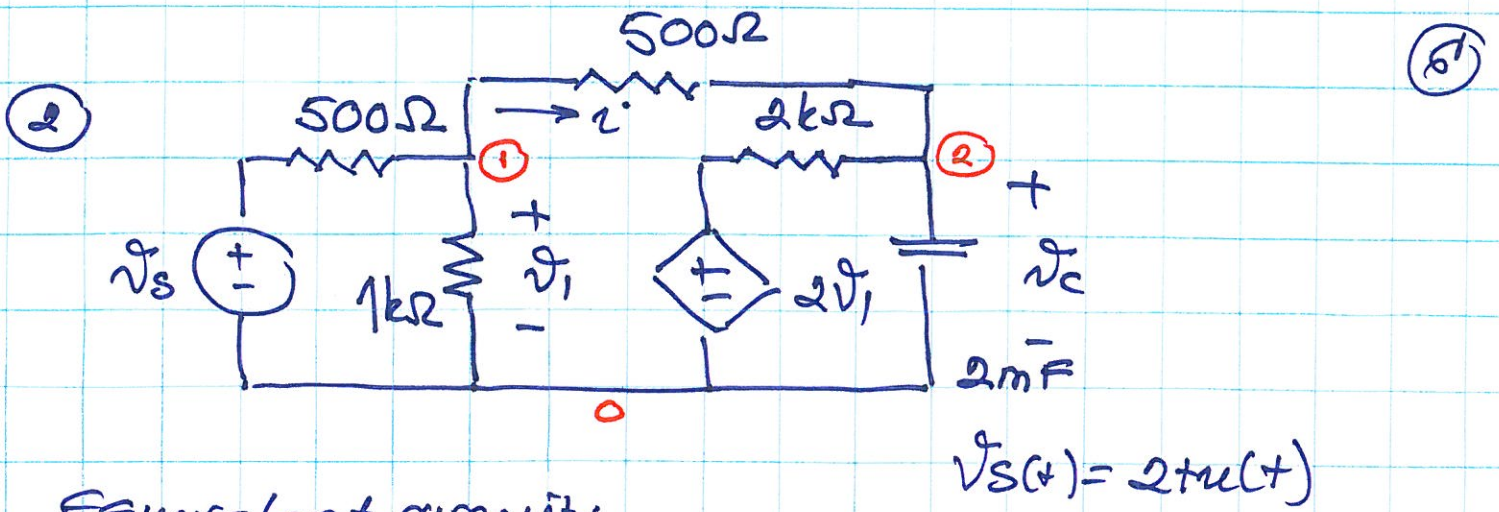
Note that in this case the rest of the circuit is open.




Equivalent circuit:

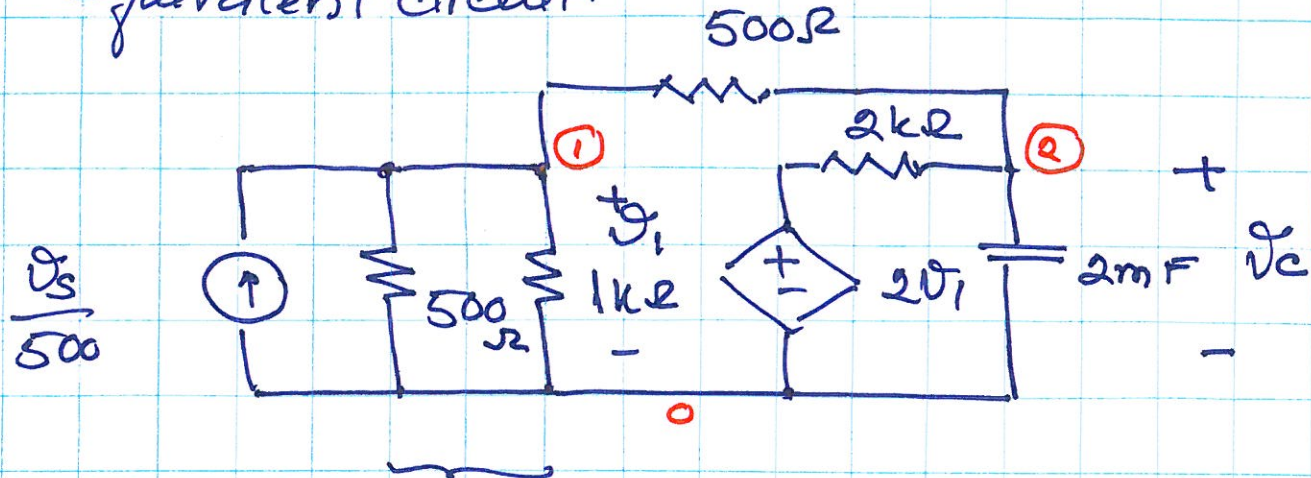
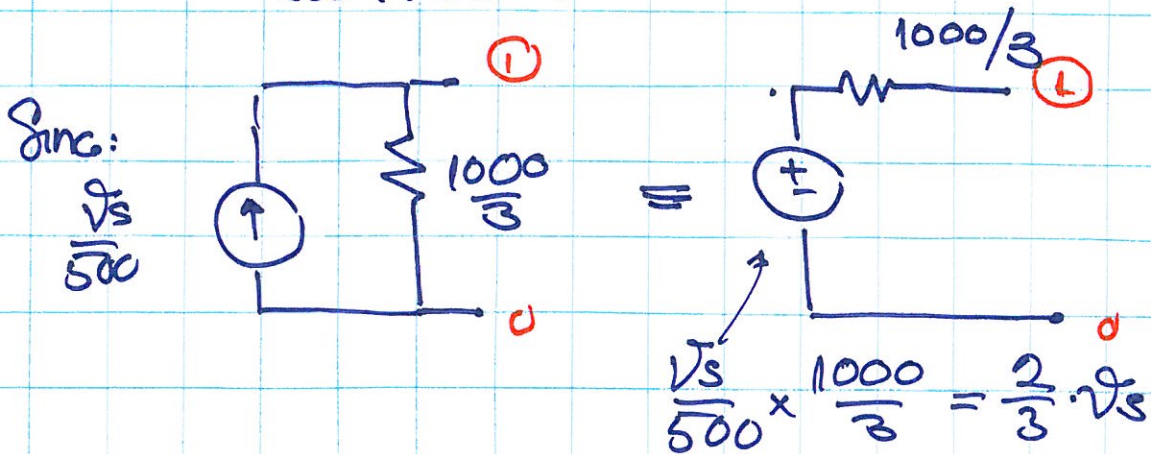
$$R_e = \frac{500 \times 1000}{500 + 1000} ; R_e = \frac{1000}{3} \Omega$$



The circuit becomes:

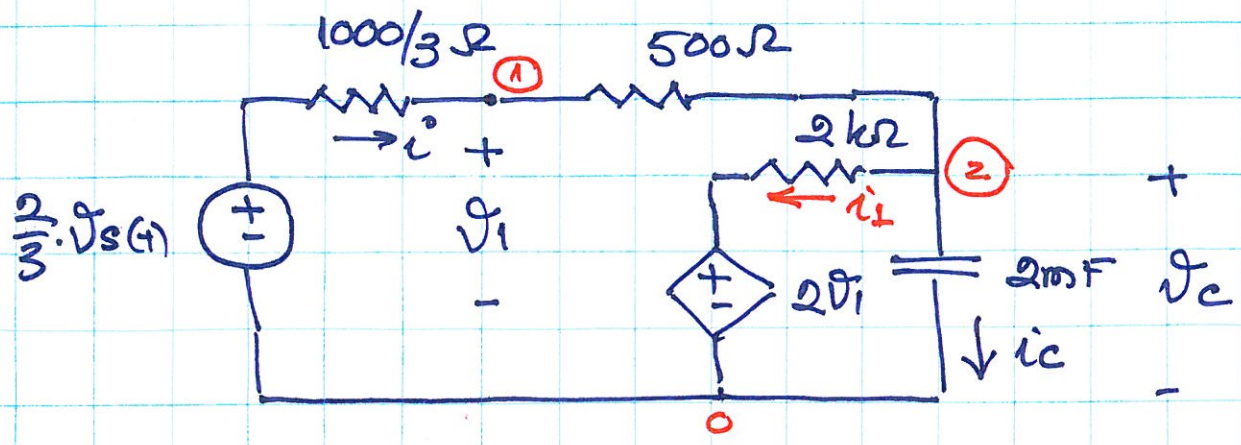

KVL:

$$\frac{2}{3} \cdot V_s(t) - \frac{1000}{3} \cdot i^0 - 500 \cdot i - V_c = 0$$

$$2V_1 + 2 \times 10^3 \cdot i_1 - V_c = 0$$

$$i_1 = i^0 - i_c$$

$$i_c = C \frac{dV_c}{dt}; \quad i_c = 2 \times 10^{-3} \frac{dV_c}{dt}$$

Note: $V_s(t) = t u(t)$

Hence:

$$\left(\frac{1000}{3} + 500\right) \cdot i^0 + V_c = \frac{2}{3} \cdot t u(t)$$

$$2V_c + 2 \times 10^3 \cdot (i - i_c) - V_c = 0$$

$$i_c = 2 \times 10^{-3} \frac{dV_c}{dt}$$

Note that: $V_1 - 500 \times i - V_c = 0$

Hence: $V_1 = 500i + V_c$

Then:

$$\frac{2500}{3} \cdot i + V_c = \frac{2}{3} \cdot t \quad u(t) = 1 \text{ for } t \geq 0$$

$$2 \cdot (500i + V_c) + 2 \times 10^3 (i - i_c) - V_c = 0$$

From the 1st eqn:

$$i^0 = \frac{3}{2100} \cdot \left(\frac{2}{3}t - v_c \right)$$

Equation 2 can be arranged as:

$$(2 \times 100 + 2 \times 10^3) i^0 + 2 \cdot v_c - 2 \times 10^3 \cdot i_c - v_c = 0$$

$$3000 \cdot i^0 + v_c - 2 \times 10^3 \cdot 2 \times 10^{-3} \frac{dv_c}{dt} = 0$$

or: $3000 \times \frac{3}{2100} \cdot \left(\frac{2}{3}t - v_c \right) + v_c - 4 \cdot \frac{dv_c}{dt} = 0$

$$-4 \frac{dv_c}{dt} + v_c \left(1 - \frac{30 \times 3}{21} \right) = - \frac{3 \times 30}{21} \times \frac{2}{3} \cdot t$$

$$-4 \frac{dv_c}{dt} - \frac{13}{5} v_c = - \frac{12}{5} t \quad /: (-4)$$

$$\frac{dv_c}{dt} + \frac{13}{20} v_c = \frac{3}{5} t$$

1st order differential eqn:

Character eqn: $s + \frac{13}{20} = 0$; $s = -\frac{13}{20}$

$$v_{ch} = k e^{-13/20 t} \quad ; \quad v_c(t) = v_{ch}(t) + v_{cp}(t)$$

Given: $v_c(0^-) = 0$; $v_c(0^+) = 0$

$v_{cp}(t) = at + b$ (Recall that: input is a ramp func.)

$\frac{dv_{cp}}{dt} = a$; Hence $a + \frac{13}{20} \cdot (at + b) = \frac{3}{5} t$
from DAE:

(9)

$$a + \frac{13}{20} \cdot at + \frac{13}{20} b = \frac{3}{5} t \quad \forall t$$

$$a + \frac{13}{20} b = 0$$

$$\frac{13}{20} a = \frac{3}{5}; \quad a = \frac{12}{13}$$

$$\frac{13}{20} b = -a; \quad b = -\frac{20}{13} \times \frac{12}{13}$$

$$b = -\frac{240}{169}$$

$$v_{cp}(t) = \frac{12}{13} t - \frac{240}{169}$$

$$v_c(t) = k e^{-13/20 t} + \frac{12}{13} t - \frac{240}{169}$$

$$v_c(0+) = k - \frac{240}{169}; \quad v_c(0+) = 0; \quad k = \frac{240}{169}$$

$$i_c(t) = \left(\frac{240}{169} \cdot e^{-\frac{13}{20} t} + \frac{12}{13} t - \frac{240}{169} \right) \mu(t)$$


Current $i(t)$: through the 500Ω resistor:

$$i = \frac{3}{2500} \cdot \left(\frac{2}{3} t - v_c \right)$$

$$i = \frac{3}{2500} \times \frac{2}{3} \cdot t - \frac{3}{2500} \times \left(\frac{240}{169} e^{-13/20 t} + \frac{12}{13} t - \frac{240}{169} \right)$$


$$i = -\frac{1}{13 \times 250} \cdot t - \frac{36}{125 \times 169} \cdot e^{-13/20 t} + \frac{36}{125 \times 169}$$

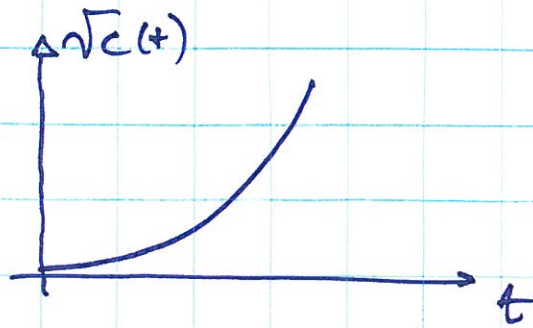At $t=0$: $v_c(0+) = 0$
 $t \rightarrow \infty$ $v_c(t) \rightarrow \infty$




At $t=0$: $i_c(0+) = 0$ (From the solution for $i_c(t)$)

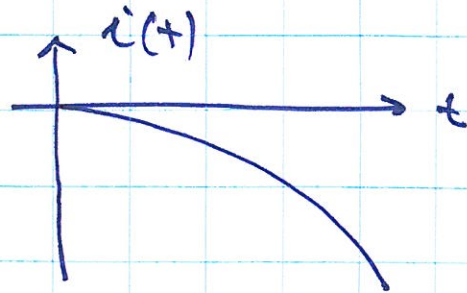$t \rightarrow \infty$ $i_c(t) \rightarrow -\infty$



3) Switch re position A:

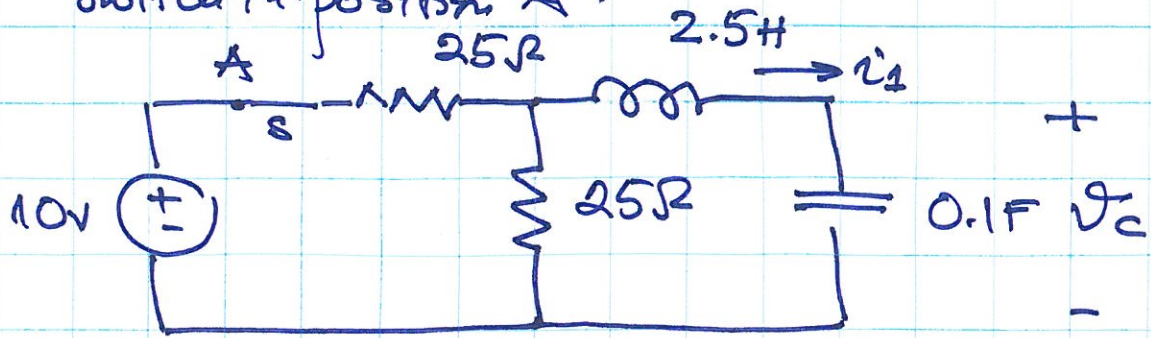


After a long time: $i_L(0^-) = 0$ (capacitor is open)

$$V_C(0^-) = \frac{10}{25+25} \times 25$$


voltage across the 25Ω resistor

hence: $i_L(0^+) = 0$ A
 $V_C(0^+) = 5$ V

Switch re position B:

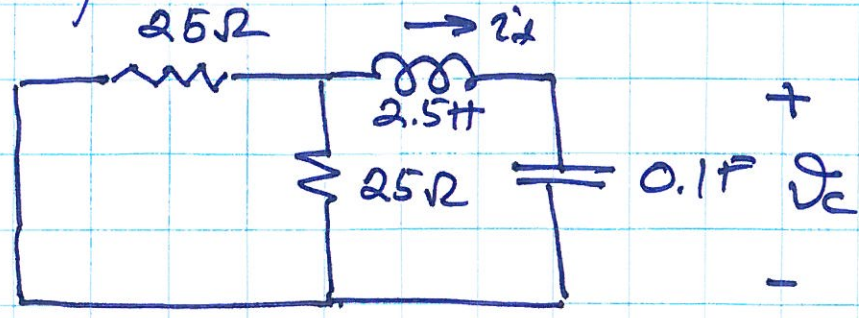

Equivalent circuit:

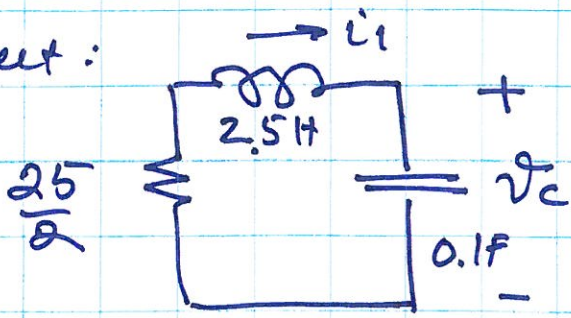

This is a second order circuit? (series RLC connect)

KVL:

$$\frac{25}{2} \times i + v_L + v_C = 0$$

$$v_L = L \frac{di}{dt} \quad ; \quad v_L = 2.5 \times \frac{di}{dt}$$

$$i = C \frac{dv_C}{dt} \quad i = 0.1 \cdot \frac{dv_C}{dt}$$

Hence:
$$\frac{25}{2} \times 0.1 \cdot \frac{dv_C}{dt} + 2.5 \cdot \frac{di}{dt} + v_C = 0$$

$$i = 0.1 \cdot \frac{dv_C}{dt}$$

OR:

$$\left. \begin{aligned} 1.25 \cdot \frac{dv_C}{dt} + 2.5 \cdot \frac{di}{dt} + v_C &= 0 \\ 0.1 \frac{dv_C}{dt} - i &= 0 \end{aligned} \right\}$$

Substitute $i = 0.1 \cdot \frac{dv_C}{dt}$ into the 1st equation:

$$1.25 \cdot \frac{dv_C}{dt} + 2.5 \cdot \left(0.1 \cdot \frac{d^2v_C}{dt^2} \right) + v_C = 0$$

$$0.25 \cdot \frac{d^2v_C}{dt^2} + 1.25 \cdot \frac{dv_C}{dt} + v_C = 0$$

Characteristic equation:

$$0.25s^2 + 1.25s + 1 = 0 \quad / \cdot 4$$

$$s^2 + 5s + 4 = 0$$

$$(s+1)(s+4) = 0$$

$$s_1 = -1$$

$$s_2 = -4$$

$$v_C(t) = k_1 e^{-t} + k_2 e^{-4t}$$

$$i(t) = k_3 e^{-t} + k_4 e^{-4t}$$

Note: $v_C(0) = 0$
(no external sources)

Find constants:

$$V_c(0) = 5$$

$$i_L(0+) = 0$$

Assume: $k_1 + k_2 = 5$
 $k_3 + k_4 = 0$

Note: $\frac{dv_c}{dt} = k_1(-1)e^{-t} + k_2(-4)e^{-4t}$

$$\frac{di_L}{dt} = k_3(-1)e^{-t} + k_4(-4)e^{-4t}$$

at $t=0+$: $\left. \frac{dv_c}{dt} \right|_{0+} = -k_1 - 4k_2$

$$\left. \frac{di_L}{dt} \right|_{0+} = -k_3 - 4k_4$$

From the differential equation:

$$\left. \begin{aligned} 1.2r \cdot \frac{dv_c}{dt} + 2.5 \cdot \frac{di_L}{dt} + v_c &= 0 \\ 0.1 \cdot \frac{dv_c}{dt} - i_L &= 0 \end{aligned} \right\}$$

At $t=0+$:

$$1.2r \cdot (-k_1 - 4k_2) + 2.5 \cdot (-k_3 - 4k_4) + 5 = 0$$

$$0.1 \cdot (-k_1 - 4k_2) - 0 = 0$$

or:

$$1.2r(k_1 + 4k_2) + 2.5(k_3 + 4k_4) = 5$$

$$-k_1 - 4k_2 = 0$$

Equations to be solved:

$$k_1 + k_2 = 5$$

$$k_3 + k_4 = 0$$

$$1.25 \cdot (k_1 + 4k_2) + 2.5(k_3 + 4k_4) = 5$$

$$k_1 + 4k_2 = 0$$

From the 1st and 4th equation:

$$k_1 + k_2 = 5$$

$$k_1 + 4k_2 = 0 \Rightarrow k_2 - 4k_2 = 5$$

$$k_2 = -\frac{5}{3}$$

$$k_1 = \frac{20}{3}$$

Also: $k_3 + k_4 = 0$

$$1.25 \cdot (k_1 + 4k_2) + 2.5 \cdot (k_3 + 4k_4) = 5$$

note from the previous calculation that $k_1 + 4k_2 = 0$

Hence:

$$k_3 + k_4 = 0$$

$$2.5 \cdot (k_3 + 4k_4) = 5 \quad \text{or} \quad k_3 + k_4 = 0$$

$$k_3 + 4k_4 = 2$$

$$3k_4 = 2; \quad k_4 = \frac{2}{3}$$

$$k_3 = -\frac{2}{3}$$

Finally: $v_c(t) = \left(\frac{20}{3} e^{-t} - \frac{5}{3} e^{-4t} \right) u(t)$


$$i(t) = \left(-\frac{2}{3} e^{-t} + \frac{2}{3} e^{-4t} \right) u(t)$$

At $t \rightarrow \infty$

$$v_c(t) = 0$$

$$i(t) = 0 \quad \text{as expected.}$$

4

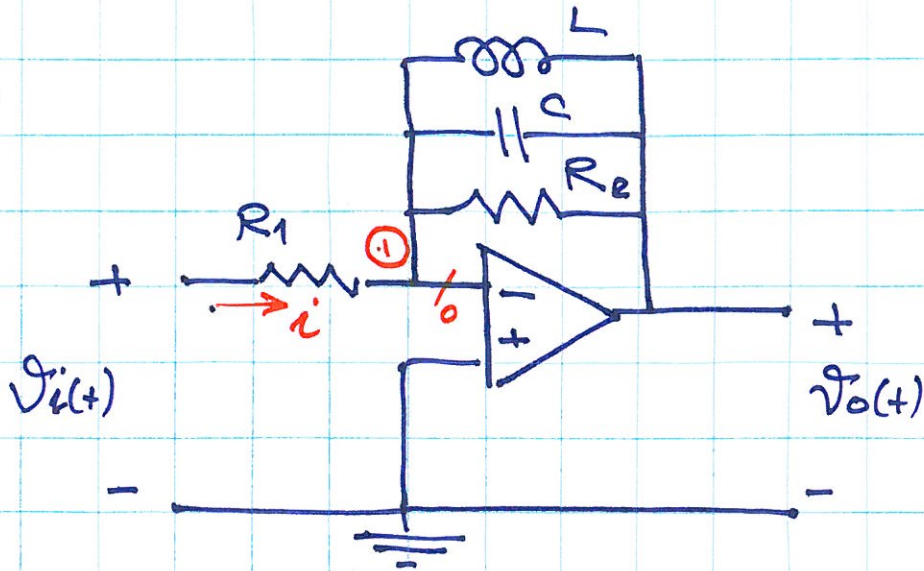

The op-amp is ideal. Hence:

$$V_i = 0$$

Phasor:


$$V_i = 0$$

$$V_i - R_1 \cdot I - V_i = 0$$

or

$$I = \frac{V_i}{R_1}$$

V_i = phasor of $V_i(t)$

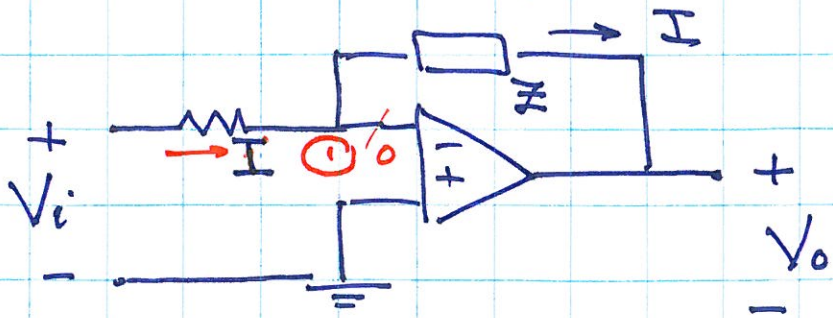

$$Z = \frac{1}{s} ; Y = \frac{1}{j\omega L} + j\omega C + \frac{1}{R_2}$$

(admittance of three parallel branches)

$$V_o + Z \cdot I = 0$$

$$V_o = -Z \cdot \frac{V_i}{R_1}$$

$$V_o = -\frac{1}{Y} \cdot \frac{V_i}{R_1}$$

$$V_o = -\frac{1}{\frac{1}{j\omega L} + j\omega C + \frac{1}{R_2}} \times \frac{1}{R_1} \times V_i$$

$$V_o = -\frac{j\omega L \times R_2}{R_2 - R_2 \cdot \omega^2 LC + j\omega L} \times \frac{1}{R_1} \cdot V_i$$

$$V_o = -\frac{R_2}{R_1} \cdot \frac{j\omega L}{R_2(1 - \omega^2 LC) + j\omega L} \cdot V_i$$

Ratio: $\frac{V_o}{V_i} = -\frac{R_2}{R_1} \cdot \frac{j\omega L}{R_2(1 - \omega^2 LC) + j\omega L}$

if $\omega^2 LC = 1$ or $\omega = 1/\sqrt{LC}$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \cdot \frac{j\omega L}{j\omega L} \quad \text{or} \quad \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

Then: $V_o = -\frac{R_2}{R_1} \cdot V_i$ phasors

or $V_o(t) = -\frac{R_2}{R_1} \cdot V_i(t)$ Time domain