

SIMON FRASER UNIVERSITY
SCHOOL OF ENGINEERING SCIENCE

ENSC 220
ELECTRIC CIRCUITS I

Final Examination (Makeup)
February 4, 1999

Attempt all four problems. Problems are equally weighted.

1. For the circuit shown in Fig. 1 assume that $k = 2/3$.
 - Find the Thévenin's equivalent circuit between the terminals $a - b$.
 - For what value of k is the open-circuit voltage zero?
 - Determine R_{th} for that value of k .
2. The circuit shown in Fig. 2 has an ideal op-amp.
 - Obtain the differential equations for $v_{out}(t)$ by writing nodal analysis equations.
 - Determine the response to $v_{in}(t) = 1u(t)$, assuming that $v_C(0_-) = 0$.
 - What would be an appropriate name for this circuit?
3. For the circuit shown in Fig. 3:
 - Write the state equations.
 - Find the value of the negative resistance R required to generate sinusoidal oscillations with constant amplitude.
4. The circuit shown in Fig. 4 operates in a sinusoidal steady-state at the radian frequency $\omega = 1$ rad/sec.
 - Find the Thévenin's voltage circuit between the terminals $a - b$ by writing mesh equations.
 - Find the Thévenin's impedance between the terminals $a - b$ by writing nodal equations.

