

SIMON FRASER UNIVERSITY
SCHOOL OF ENGINEERING SCIENCE

Fall 2008
ENSC 220: ELECTRIC CIRCUITS I

Midterm Examination
Thursday, October 23, 2008

Duration: 110 minutes. Attempt all problems. Questions are not equally weighted. Closed book and closed notes. Calculators, PDAs, laptops, and wireless phones are not permitted.

1. (10 points)

In the circuit shown in Figure 1, find the power absorbed by the load R_L . Use an appropriate unit for the calculated power.

2. (20 points)

For the circuit shown in Figure 2 with $I_1 = 0.4A$:

- Write nodal equations.
- Find voltages V_A , V_B , and V_x .

3. (20 points)

In the circuit shown in Figure 3 with $V_{s1} = 250V$ and $I_{s2} = 0.75A$:

- Write mesh equations.
- Find I_x .
- Find the power delivered by all the sources in the circuit.

4. (20 points)

The operational amplifier shown in Figure 4 is ideal.

- Find the output voltage V_o .
- Find a relationship among resistors such that the output is proportional to the difference of the two input voltages. This circuit may be used as a difference amplifier.

5. (30 points)

For the circuit shown in Figure 5:

- Find the Thévenin's equivalent for the circuit seen left of R_L .
- Determine the value of R_L required for maximum power transfer.
- Determine maximum power that can be absorbed by R_L .

Figure 1.

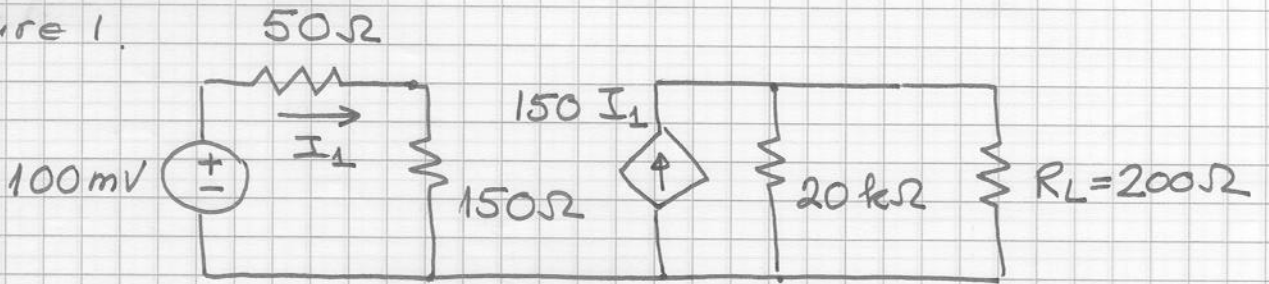


Figure 2.

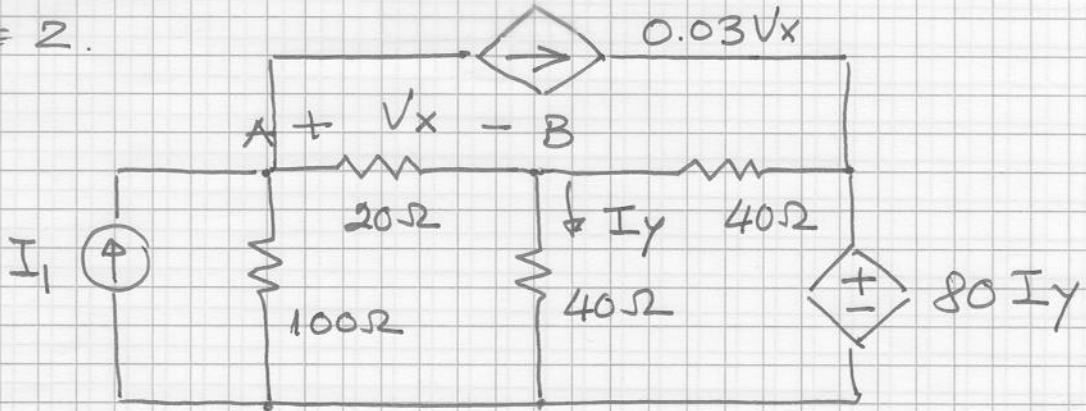


Figure 3.

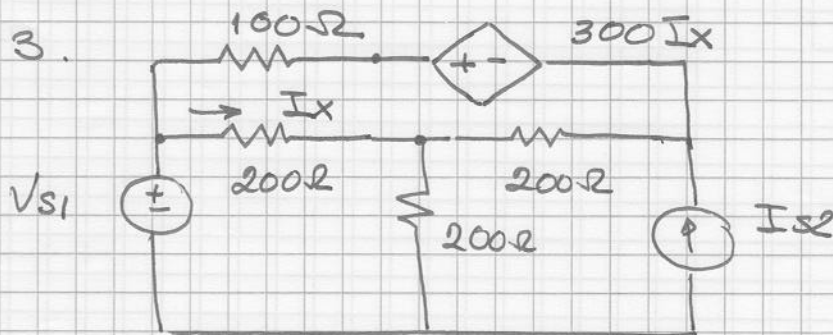


Figure 4.

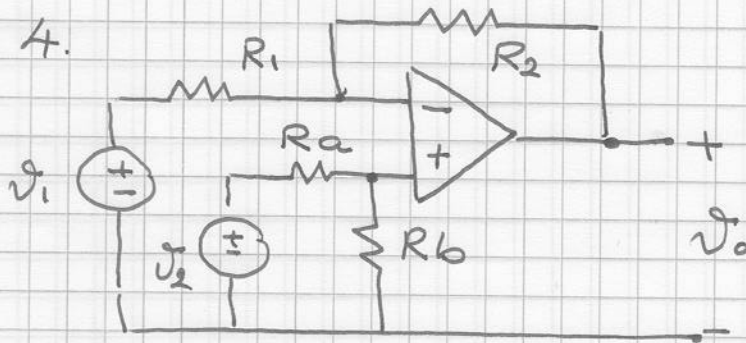


Figure 5.

