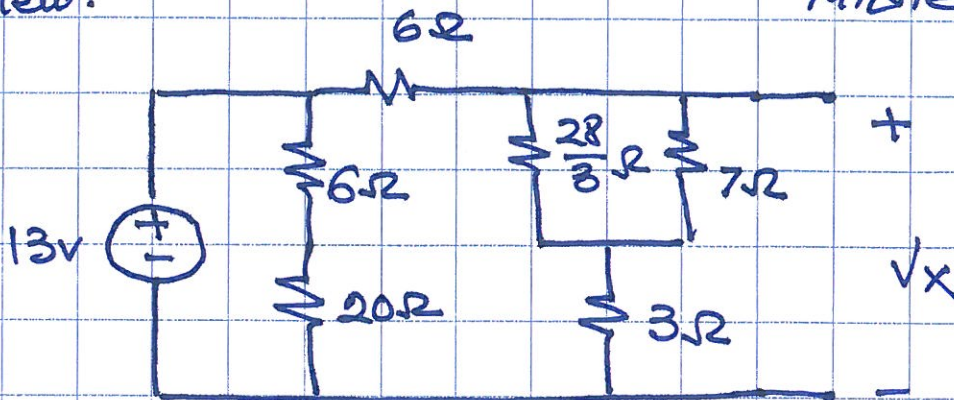


Problem:


①

①



$$V_x = ?$$

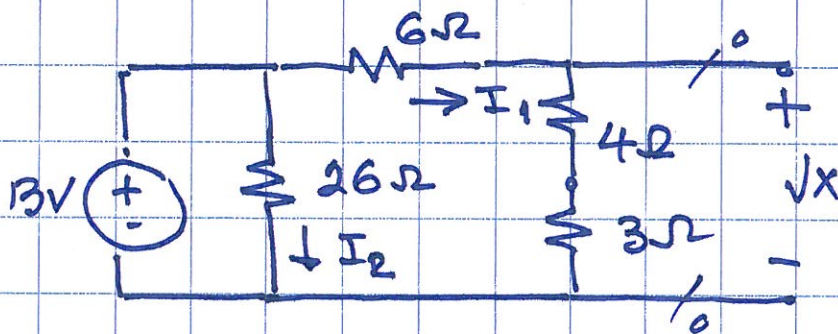Simplify the circuit by combining resistors connected in series and in parallel:



$$\text{Where: } 6\Omega + 20\Omega = 26\Omega$$

$$\begin{aligned} \frac{\frac{28}{3} \times 7}{\frac{28}{3} + 7} &= \frac{28 \times 7}{28 + 3 \times 7} \\ &= \frac{28 \times 7}{49} \\ &= 4\Omega \end{aligned}$$

$$\text{Note that: } I_1 = \frac{13}{6+4+3}; I_1 = 1\text{A}$$


$$V_x = (4+3) \times I_1; V_x = 7 \times 1; V_x = 7\text{V}$$



Problem:

(2)

(2)

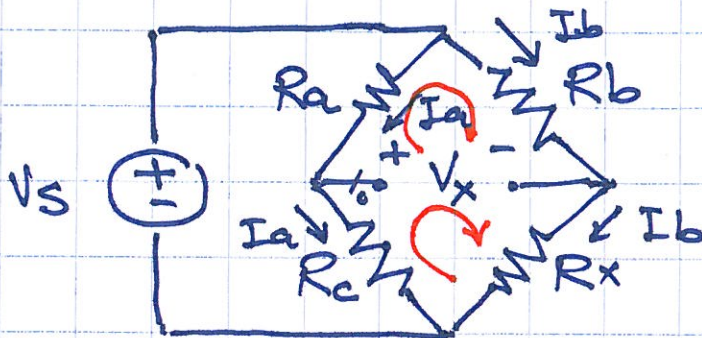

$R_x = ?$  if the bridge is balanced  
 $V_x = 0$

KVL for the top mesh:

$$R_a \cdot I_a - R_b \cdot I_b = 0 \quad (1)$$

KVL for the bottom mesh:

$$R_c \cdot I_a - R_x \cdot I_b = 0 \quad (2)$$

Note: No current flows through the terminals where we measure  $V_x$

Hence, based on KCL:

$$I_{R_a} = I_{R_c}$$

$$I_{R_b} = I_{R_x}$$

Hence,  $R_a I_a = R_b I_b$  (3)

$$R_c I_a = R_x I_b \quad (4)$$

Dividing (3) and (4) gives:


$$\frac{R_a}{R_c} = \frac{R_b}{R_x} \quad \text{or} \quad R_x = \frac{R_a R_b}{R_c}$$



Problem:

3

3

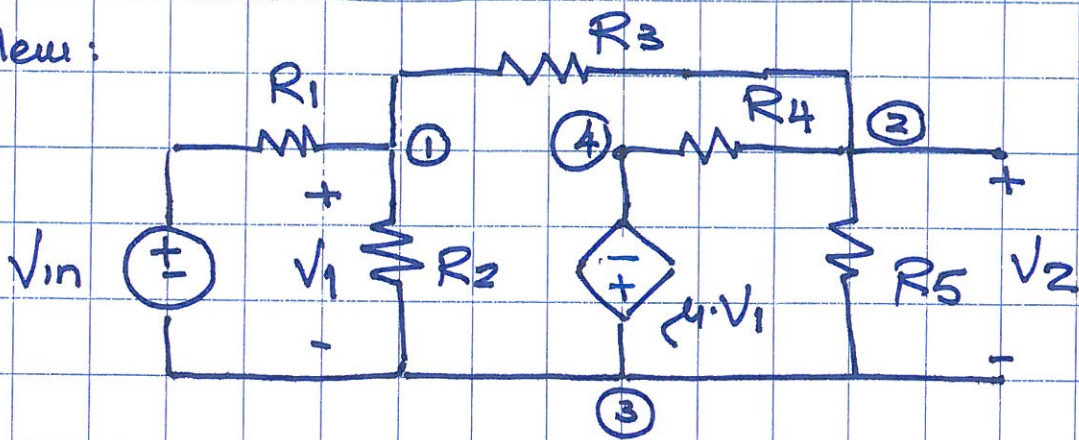

Write 2 nodal equations:

$$\textcircled{1} \quad \frac{v_1 - v_{in}}{R_1} + \frac{v_1}{R_2} + \frac{v_1 - v_2}{R_3} = 0 \quad (1)$$

$$\textcircled{2} \quad \frac{v_2 - v_1}{R_3} + \frac{v_2 - v_4}{R_4} + \frac{v_2}{R_5} = 0 \quad (2)$$

Note that  $v_4 = -4 \cdot v_1$

$$\text{Hence, } v_1 \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{1}{R_3} \cdot v_2 = \frac{1}{R_1} \cdot v_{in} \quad (3)$$

$$v_2 \cdot \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) - \frac{1}{R_3} \cdot v_1 - \frac{1}{R_4} \cdot (-4 \cdot v_1) = 0 \quad (4)$$

$$\text{Or: } v_1 \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{1}{R_3} \cdot v_2 = \frac{1}{R_1} \cdot v_{in}$$

$$-v_1 \cdot \left( \frac{1}{R_3} - 4 \cdot \frac{1}{R_4} \right) + v_2 \cdot \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) = 0$$

$$\text{Conductance matrix: } \begin{pmatrix} G_1 + G_2 + G_3 & -G_3 \\ -G_3 + 4 \cdot G_4 & G_3 + G_4 + G_5 \end{pmatrix}$$



If  $\mu = 0$  (no controlled source)

Conductance matrix is:

$$\begin{pmatrix} G_1 + G_2 + G_3 & -G_3 \\ -G_3 & G_3 + G_4 + G_5 \end{pmatrix}$$


Properties:

- symmetric
- all diagonal elements are positive
- all off-diagonal elements are negative.

Problem:

5

4


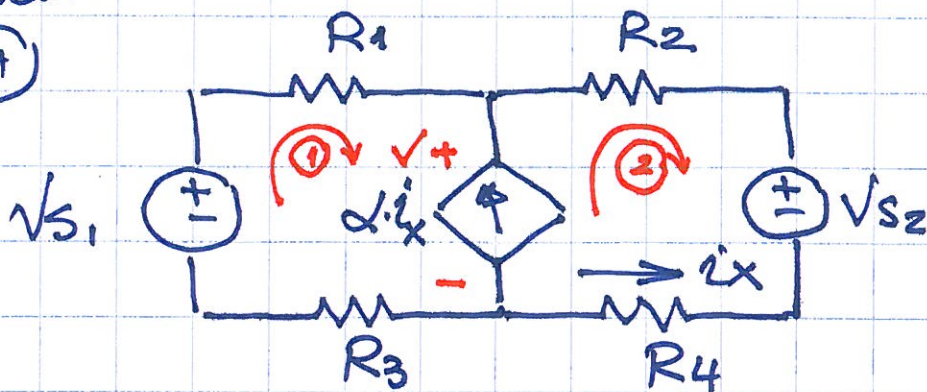


Write two mesh equations:

Mesh currents:

$$(1) R_1 \cdot j_1 + R_3 \cdot j_1 + V - V_{s1} = 0$$
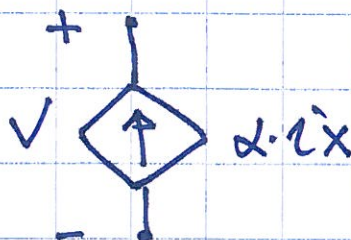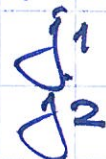
$$(2) R_2 \cdot j_2 + R_4 \cdot j_2 - V + V_{s2} = 0$$



Hence:

$$(R_1 + R_3) \cdot j_1 + V = V_{s1} \quad (3)$$

$$(R_2 + R_4) \cdot j_2 - V = -V_{s2} \quad (4)$$

Note that  $j_2 - j_1 = \alpha \cdot i_x$   
 $i_x = -j_2$

Hence, (5)  $(R_1 + R_3) \cdot j_1 + V = V_{s1}$

(6)  $(R_2 + R_4) \cdot j_2 - V = -V_{s2}$

(7)  $j_2 - j_1 = \alpha \cdot (-j_2)$  or  $(1 + \alpha) \cdot j_2 - j_1 = 0$



Adding (5) and (6) to eliminate  $V$  gives:

(6)

$$(8) \quad (R_1 + R_3) \cdot j_1 + (R_2 + R_4) \cdot j_2 = V_{s1} - V_{s2}$$

$$(9) \quad -j_1 + (1 + \alpha) \cdot j_2 = 0$$

Resistance matrix:

$$\begin{pmatrix} R_1 + R_3 & R_2 + R_4 \\ -1 & 1 + \alpha \end{pmatrix}$$

If  $\alpha = 0$ , current controlled current source is removed

$$j_1 = j_2$$

matrix degenerates to:

$$(R_1 + R_2 + R_3 + R_4) \cdot j_1 = V_{s1} - V_{s2}$$

Properties:

- symmetric
- all diagonal elements positive
- all off diagonal elements positive or negative depending on the orientation of mesh currents

Solution:

$$(30 + 20) j_1 + (270 + 80) j_2 = 225 - 15$$

$$-j_1 + (1 - 0.5) j_2 = 0$$



7

$$50j_1 + 350j_2 = 210$$

$$-j_1 + 0.5j_2 = 0$$

$$\text{or: } j_2 = 2j_1$$

Then,

$$50j_1 + 350 \cdot 2j_1 = 210$$

$$750j_1 = 210$$

$$j_1 = \frac{210}{750}$$

$$j_1 = \frac{4}{25} \text{ A}$$

$$j_2 = \frac{14}{25} \text{ A}$$