

SIMON FRASER UNIVERSITY  
SCHOOL OF ENGINEERING SCIENCE


ENSC 220  
ELECTRIC CIRCUITS I

Midterm Examination No. 1  
October 14, 1998


*Attempt all four problems. Problems are equally weighted.*

1. Derive the expression relating the voltage to the current at the terminals A-B. Plot the result.
2. Find the Thévenin's equivalent at the terminals x-y. Find the maximum power that can be delivered to an appropriate resistor  $R_x$  connected across x-y.
3. Find the voltage and the current in the diode if its v-i characteristics is as shown. What would be your answer if the diode was modeled as an ideal on-off switch?
4. Solve only one of the two cases:
  - (a) The waveform of the current in a 2H inductor is shown. Sketch to scale the voltage  $v$  across the inductor. What is the source voltage  $v_s$  that can produce such current. Show your equations.
  - (b) The waveform of the current (in  $\mu\text{A}$ ) in a 2  $\mu\text{F}$  capacitor is shown. Sketch to scale the voltage  $v$  across the capacitor. What is the source voltage  $v_s$  that can produce such current. Show your equations.



1.

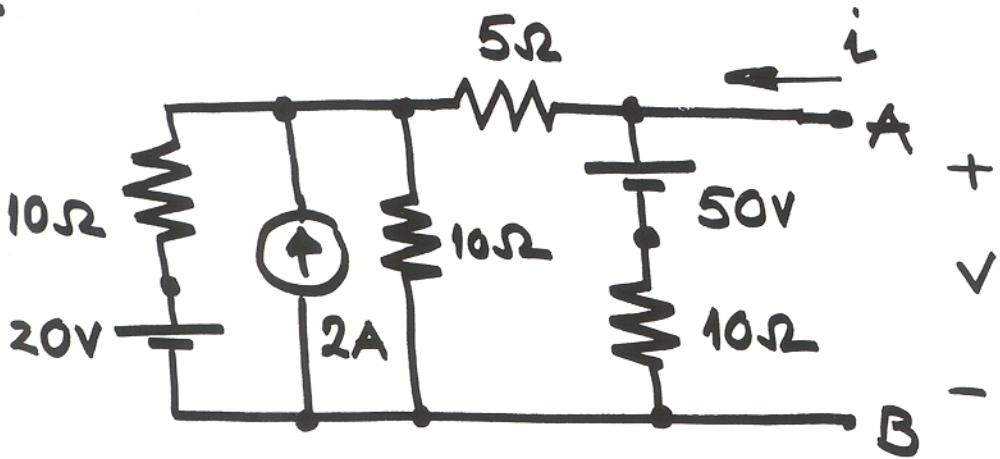



2.

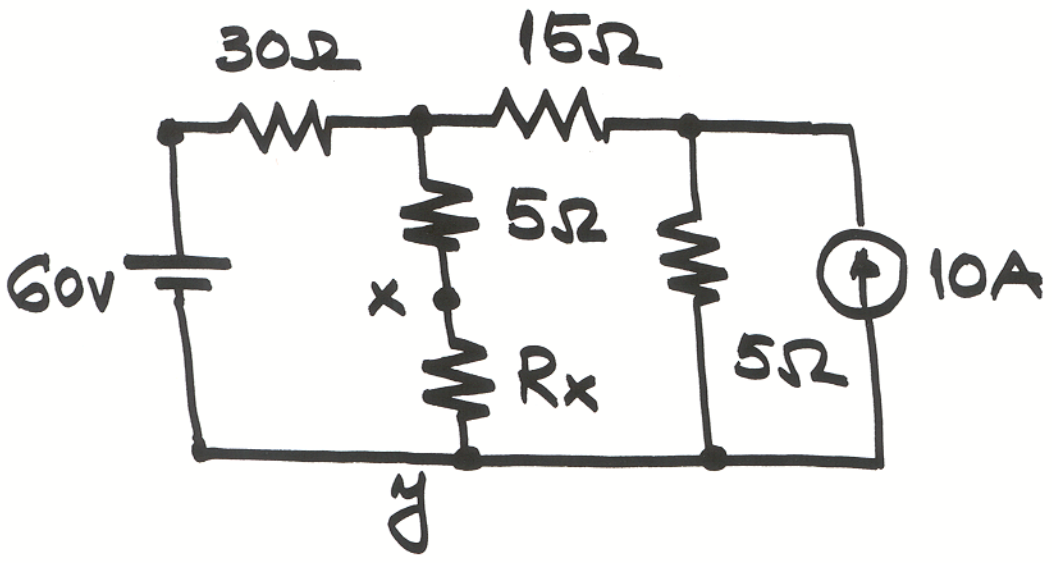

3.

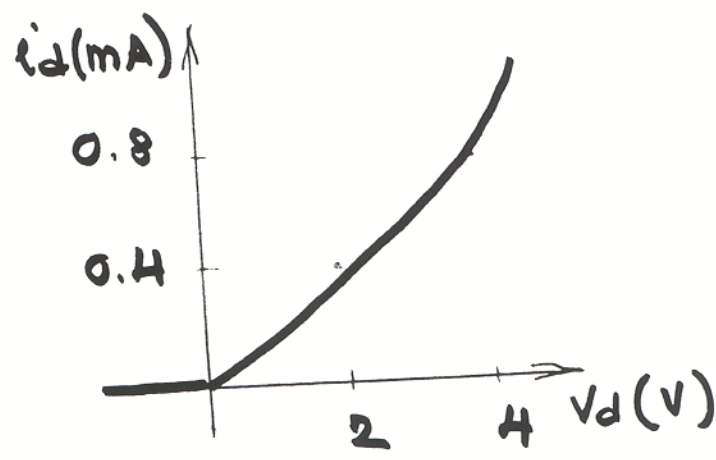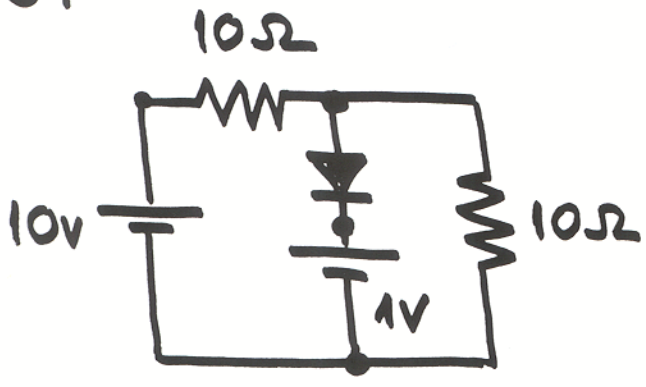

4(a)

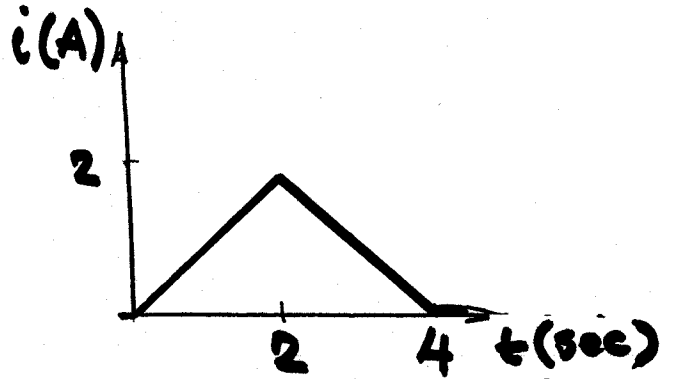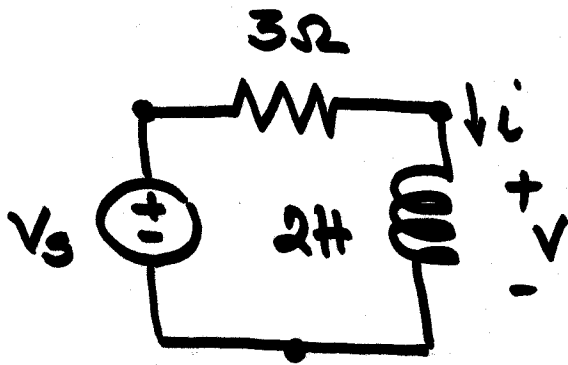

4(b)

