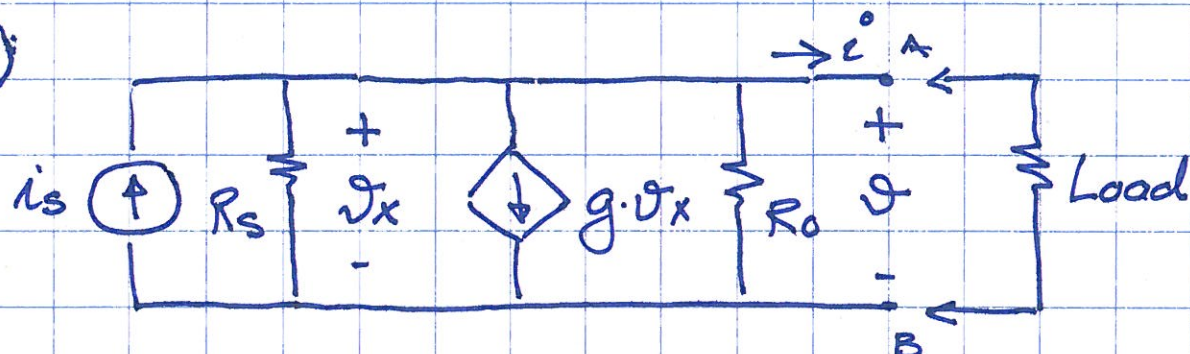


*1




$$V_{th} = ?$$

$$R_{th} = ?$$

To find V_{th} keep node A and B open and find V_{AB} :

Equivalent circuit

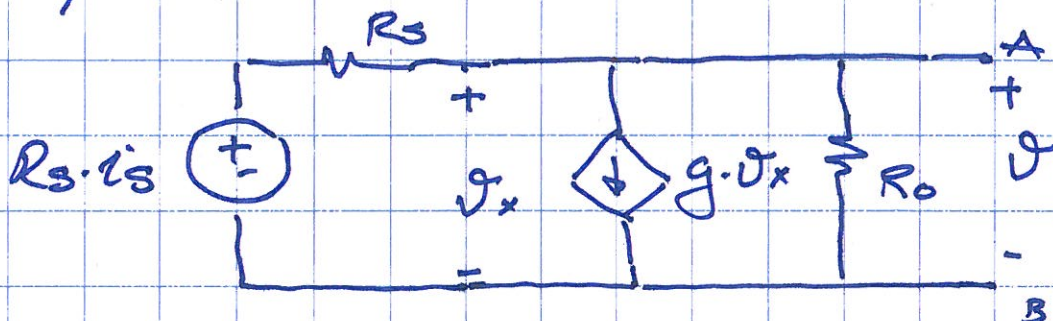

Node equation for node A:

$$\frac{v_A - R_s \cdot i_s}{R_s} + g \cdot v_x + \frac{v}{R_o} = 0$$

Note that $v_x = v_A$; $v = v_A$

Hence,

$$\frac{v - R_s \cdot i_s}{R_s} + g \cdot v + \frac{v}{R_o} = 0$$

(2)

$$v \cdot \left(\frac{1}{R_s} + \frac{1}{R_o} + g \right) = i_s$$


$$v = \frac{i_s}{\frac{1}{R_s} + \frac{1}{R_o} + g}$$

$$\text{or: } v_{Th} = \frac{R_s \cdot R_o \cdot i_s}{R_o + R_s + g \cdot R_o \cdot R_s}$$

To find R_{Th} , apply voltage v_{AB} , disconnect the current source, and find

$$R_{Th} = \frac{v_{AB}}{-i}$$

the circuit becomes:

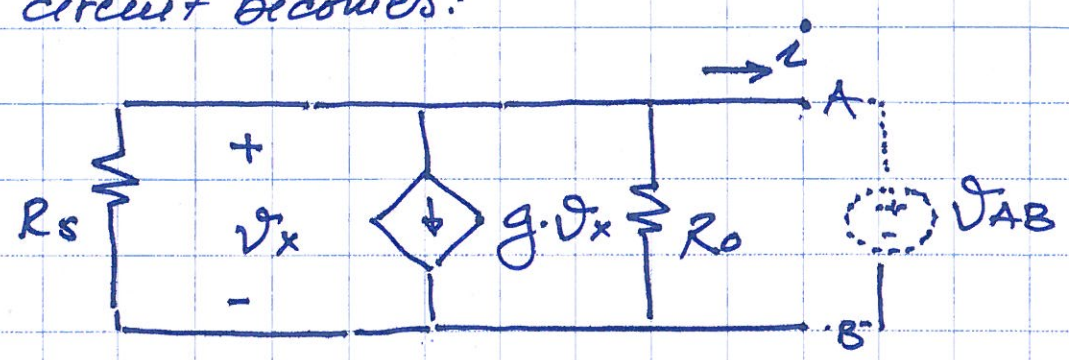

write nodal equation again to get:

$$\frac{v_{AB}}{R_s} + g \cdot v_x + \frac{v_{AB}}{R_o} + i = 0$$

Note that $v_x = v_{AB}$

$$\text{Hence, } v_{AB} \left(\frac{1}{R_s} + g + \frac{1}{R_o} \right) = -i$$

Hence,

$$\frac{V_{AB}}{-i} = \frac{1}{\frac{1}{R_s} + \frac{1}{R_o} + g}$$

$$R_{Th} = \frac{1}{\frac{1}{R_s} + \frac{1}{R_o} + g}$$


or

$$R_{Th} = \frac{R_o \cdot R_s \cdot g}{R_o + R_s + g R_o \cdot R_s}$$

Another approach to find R_{Th} is to find the Norton equivalent current i_N . Then,

$$R_{Th} = \frac{V_{Th}}{i_N}$$

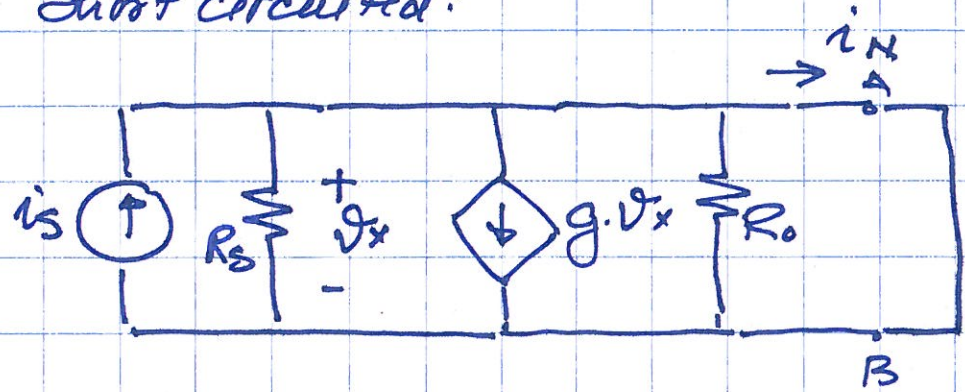Find the current i when terminals A and B are short circuited:



Nodal equation (or KCL) gives:


$$i_s - \frac{v_x}{R_s} - g \cdot v_x - i_N = 0 \quad ; \quad v_x = 0$$

Hence, $i_N = i_s$

$$R_{Th} = \frac{V_{AB}}{i_N} \quad ; \quad R_{Th} = \frac{V_{Th}}{i_N} \quad ; \quad R_{Th} = \frac{R_s \cdot R_o}{R_o + R_s + g R_o \cdot R_s}$$

4

#2

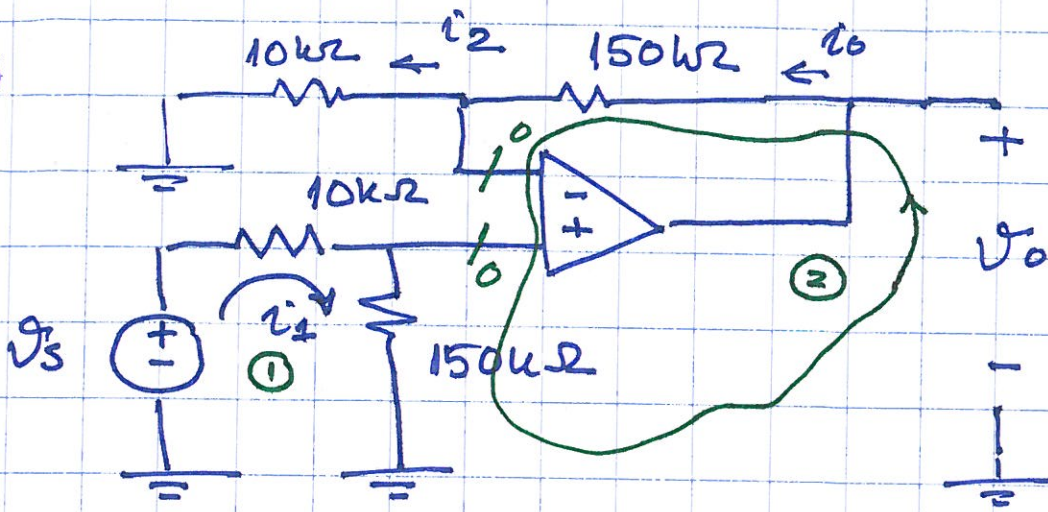

Find V_o in terms of V_s

Find i_o for $V_s = 1\text{V}$

Ideal op amp: $i_- = 0$; $i_+ = 0$; $V_+ = V_- = 0$

KVL: $V_s - 10 \times 10^3 \cdot i_1 - 150 \times 10^3 \cdot i_1 = 0$ Loop 1

$$i_1 = \frac{V_s}{160} \times 10^{-3}$$

KCL: $i_2 = i_o$

Note that $V_- = V_+$

Since $V_- = 10 \times 10^3 \cdot i_2$

$$V_+ = 150 \times 10^3 \cdot i_1$$

Then $10 \times 10^3 \cdot i_2 = 150 \times 10^3 \cdot i_1$; $i_2 = 15 \cdot i_1$

and $i_o = 15 \cdot i_1$

KVL for loop 2:

$$V_o - 150 \times 10^3 \cdot i_o - 150 \times 10^3 \cdot i_1 = 0$$

$$V_o = 150 \times 10^3 (i_o + i_1)$$

5

$$v_o = 150 \times 10^3 \cdot (15i_1 + 14)$$

Recall that $i_1 = \frac{v_s}{160} \times 10^{-3}$

Hence, $v_o = 150 \cdot 10^3 \cdot 16 \cdot \frac{v_s}{160} \cdot 10^{-3}$

$$v_o = 15 \cdot v_s \quad (\text{gain} = 15)$$

If $v_s = 1V$


then $i_1 = \frac{1 \times 10^{-3}}{160}$

$$i_o = 15 \cdot i_1$$

$$i_o = \frac{15}{160} \times 10^{-3} \text{ A} \quad ; \quad i_o = \frac{3}{32} \times 10^{-3} \text{ A}$$

$$i_o = \frac{3}{32} \text{ mA}$$

or $i_o = 93.75 \mu\text{A}$

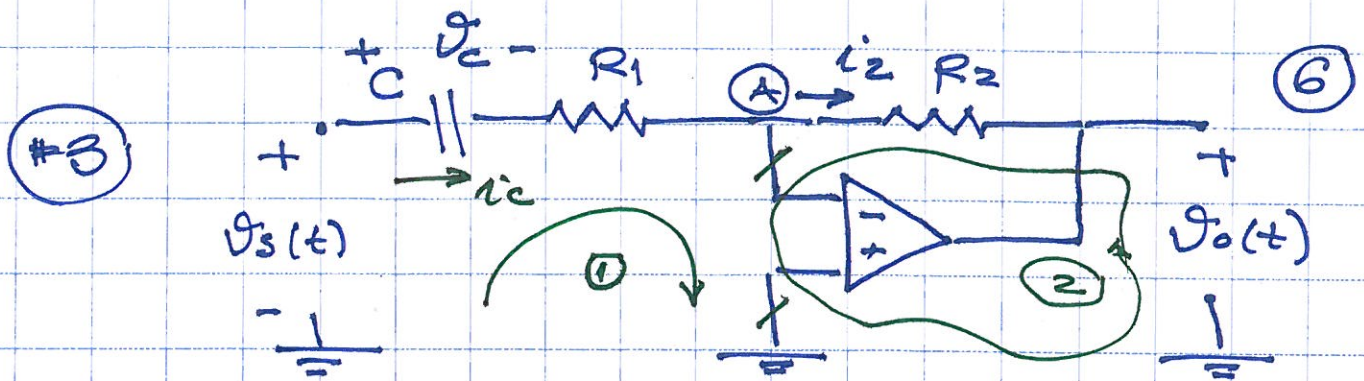

Find relationship between $v_o(t)$ and $v_s(t)$.

KVL for loop 1:

$$v_s(t) - v_c(t) - v_{R_1}(t) = 0$$

or

$$v_s - v_c - v_{R_1} = 0$$

$$v_{R_1} = R_1 \cdot i_c$$

$$i_c = C \cdot \frac{dv_c}{dt}$$

Hence, $v_c + R_1 \cdot C \cdot \frac{dv_c}{dt} = v_s$

Let us express $v_o(t)$ in terms of $v_c(t)$:

KVL for loop 2:

$$v_o(t) + R_2 \cdot i_2 = 0 ;$$

KCL for node A: $i_c - i_2 = 0 ; i_2 = i_c$

Hence:

$$v_o - R_2 \cdot i_c = 0 ; v_o = R_2 \cdot C \cdot \frac{dv_c}{dt}$$

From the two equations:

$$v_c + R_1 C \cdot \frac{dv_c}{dt} = v_s \quad (1)$$

we get: $v_o = R_2 C \cdot \frac{dv_c}{dt} \quad (2)$

$$V_C = \frac{1}{R_2 C} \cdot \int V_0(x) dx \quad \text{from (2)}$$

(4)

Substitute into (1):

$$\frac{1}{R_2 C} \cdot \int V_0(x) dx + R_1 C \cdot \frac{1}{R_2 C} \cdot V_0 = V_S$$

or


$$\frac{R_1}{R_2} \cdot V_0 + \frac{1}{R_2 C} \cdot \int V_0(x) dx = V_S$$

Find the derivative to avoid having an integral:

$$\frac{R_1}{R_2} \cdot \frac{dV_0}{dt} + \frac{1}{R_2 C} \cdot V_0 = \frac{dV_S}{dt}$$

PA

2

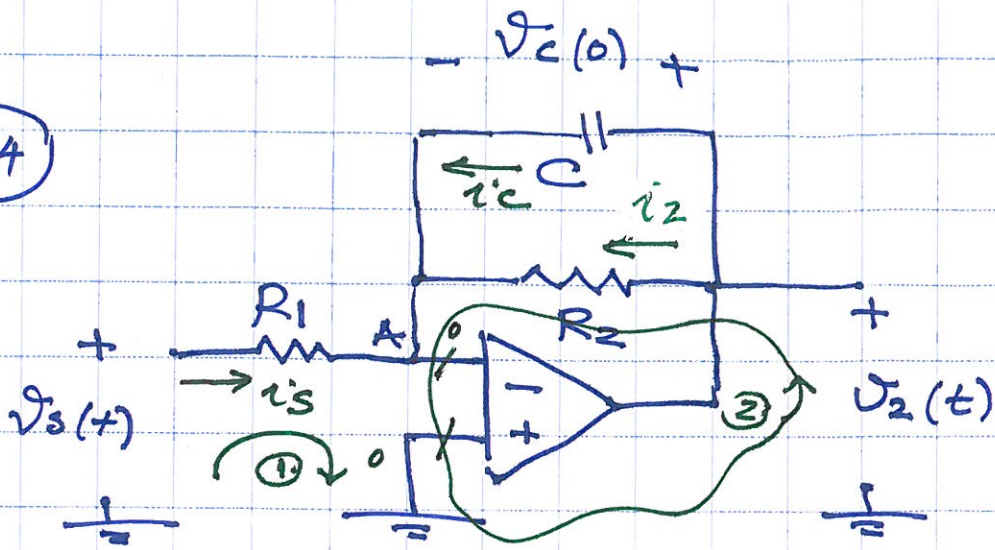

ideal op amp:
 $v_- = v_+; v_- = 0$
 $v_+ = 0$
 $i_- = 0$
 $i_+ = 0$

KVL: $v_s - R_1 \cdot i_s = 0$ Loop ①

$$i_s = \frac{1}{R_1} \cdot v_s$$

KVL: $v_2 - R_2 \cdot i_2 = 0$ Loop ②

$$i_2 = \frac{v_2}{R_2}$$

Note that: $v_c = v_2$; $i_c = \frac{1}{R_2} \cdot v_c$

KCL for node A:

$$i_s + i_c + i_2 = 0$$

Hence, $\frac{1}{R_1} \cdot v_s + i_c + \frac{1}{R_2} \cdot v_c = 0$

Since $i_c = C \frac{dv_c}{dt}$; $C \frac{dv_c}{dt} + \frac{1}{R_2} \cdot v_c = -\frac{1}{R_1} \cdot v_s$ (DAE)

9

Let $v_s(t) = 2 \cdot u(t)$

DAE becomes:

$$C \cdot \frac{dv_c}{dt} + \frac{1}{R_2} \cdot v_c = -\frac{1}{R_1} \cdot 2 \cdot u(t)$$

or

$$\frac{dv_c}{dt} + \frac{1}{CR_2} \cdot v_c = -\frac{2}{CR_1} \quad (1) \text{ for } t \geq 0$$

Solution:

$$v_{c,h}(t) = k e^{st}$$

Homogeneous solution:

$$\frac{dv_{c,h}}{dt} = k s e^{st}$$

Substituted into (1) gives:

$$k \cdot s e^{st} + \frac{1}{CR_2} \cdot k e^{st} = 0 \quad ; \quad e^{st} \neq 0$$

$k \neq 0$ (non-trivial solution)

$$s = -\frac{1}{CR_2} \quad \uparrow \text{ natural frequency}$$

$$v_{c,h} = k e^{-t/CR_2}$$

Particular solution:

$$v_{c,p}(t) = A \quad (\text{because } v_s(t) = 2u(t))$$

$$\frac{dv_{c,p}(t)}{dt} = 0$$

Hence: $0 + \frac{1}{CR_2} \cdot A = -\frac{2}{CR_1} \quad ; \quad A = -2 \frac{R_2}{R_1}$

Total solution is: $v_c(t) = k e^{-\frac{t}{CR_2}} - 2 \cdot \frac{R_2}{R_1}$

Find K from the initial conditions.

$$v_c(0^-) = V_0 ; \text{ state variable}$$

$$v_c(0^+) = V_0$$

$$V_0 = K e^{-\frac{0}{CR_2}} - 2 \cdot \frac{R_2}{R_1} ; V_0 = K - 2 \cdot \frac{R_2}{R_1}$$

$$K = V_0 + 2 \frac{R_2}{R_1}$$

Total solution is:

$$v_c(t) = \left(V_0 + 2 \frac{R_2}{R_1} \right) e^{-\frac{t}{CR_2}} - 2 \cdot \frac{R_2}{R_1} \quad \forall t \geq 0$$

It can be also written as:

$$v_c(t) = \left(\left(V_0 + 2 \frac{R_2}{R_1} \right) \cdot e^{-\frac{t}{CR_2}} - 2 \frac{R_2}{R_1} \right) \cdot u(t)$$

Recall that

$$i_s(t) = \frac{1}{R_1} \cdot v_s(t) ; i_s(t) = \frac{1}{R_1} \cdot 2 \cdot u(t)$$

$$i_s(t) = \frac{2}{R_1} \cdot u(t)$$

Graphs:

